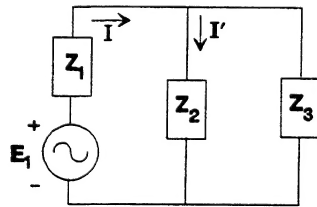


CHAPTER 18 (Odd)

1. a.




$$Z_1 = 3 \Omega \angle 0^\circ, Z_2 = 8 \Omega \angle 90^\circ, Z_3 = 6 \Omega \angle -90^\circ$$

$$Z_2 \parallel Z_3 = 8 \Omega \angle 90^\circ \parallel 6 \Omega \angle -90^\circ = 24 \Omega \angle -90^\circ$$

$$I = \frac{E_1}{Z_1 + Z_2 \parallel Z_3} = \frac{30 \text{ V} \angle 30^\circ}{3 \Omega - j24 \Omega} = 1.24 \text{ A} \angle 112.875^\circ$$
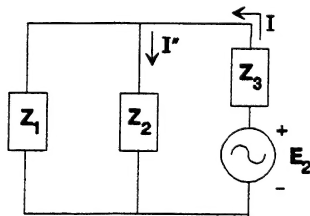
$$I' = \frac{Z_3 I}{Z_2 + Z_3} = \frac{(6 \Omega \angle -90^\circ)(1.24 \text{ A} \angle 112.875^\circ)}{2 \Omega \angle 90^\circ} = 3.72 \text{ A} \angle -67.125^\circ$$



$$Z_1 \parallel Z_2 = 3 \Omega \angle 0^\circ \parallel 8 \Omega \angle 90^\circ = 2.809 \Omega \angle 20.556^\circ$$

$$I = \frac{E_2}{Z_3 + Z_1 \parallel Z_2} = \frac{60 \text{ V} \angle 10^\circ}{-j6 \Omega + 2.630 \Omega + j0.986 \Omega} = 10.597 \text{ A} \angle 72.322^\circ$$

$$I'' = \frac{Z_1 I}{Z_1 + Z_2} = \frac{(3 \Omega \angle 0^\circ)(10.597 \text{ A} \angle 72.322^\circ)}{3 \Omega + j8 \Omega} = 3.721 \text{ A} \angle 2.878^\circ$$


$$I_{L_1} = I' + I'' = 3.72 \text{ A} \angle -67.125^\circ + 3.721 \text{ A} \angle 2.878^\circ$$

$$= 1.446 \text{ A} - j3.427 \text{ A} + 3.716 \text{ A} + j0.187 \text{ A}$$

$$= 5.162 \text{ A} - j3.24 \text{ A}$$

$$= 6.095 \text{ A} \angle -32.115^\circ$$

b.

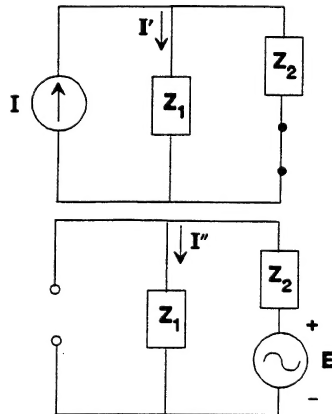

$$Z_1 = 8 \Omega \angle 90^\circ, Z_2 = 5 \Omega \angle -90^\circ$$

$$I = 0.3 \text{ A} \angle 60^\circ, E = 10 \text{ V} \angle 0^\circ$$

$$I' = \frac{Z_2 I}{Z_2 + Z_1} = \frac{(5 \Omega \angle -90^\circ)(0.3 \text{ A} \angle 60^\circ)}{+j8 \Omega - j5 \Omega} = 0.5 \text{ A} \angle -120^\circ$$

$$I'' = \frac{E}{Z_1 + Z_2} = \frac{10 \text{ V} \angle 0^\circ}{3 \Omega \angle 90^\circ} = 3.33 \text{ A} \angle -90^\circ$$

$$I_{Z_1} = I_{L_1} = I' + I''$$


$$= 0.5 \text{ A} \angle -120^\circ + 3.33 \text{ A} \angle -90^\circ$$

$$= -0.25 \text{ A} - j0.433 \text{ A} - j3.33 \text{ A}$$


$$= -0.25 \text{ A} - j3.763 \text{ A}$$

$$= 3.77 \text{ A} \angle -93.8^\circ$$

3. DC:

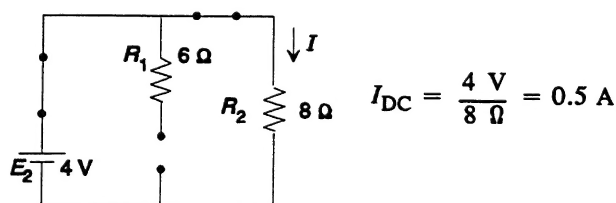


AC:

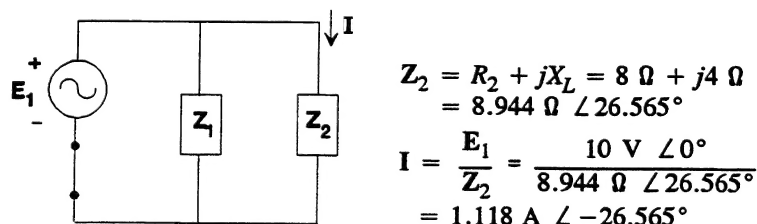

$$I = 0.5 \text{ A} + 1.118 \text{ A} \angle -26.565^\circ$$

$$i = 0.5 \text{ A} + 1.581 \sin(\omega t - 26.565^\circ)$$


5.

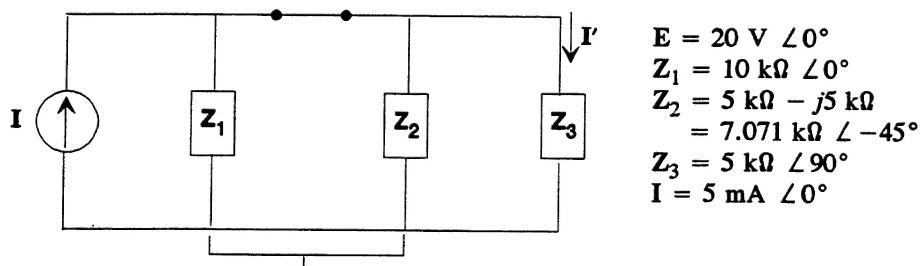

$$Z' = Z_1 \parallel Z_2 = 10 \text{ k}\Omega \angle 0^\circ \parallel 7.071 \text{ k}\Omega \angle -45^\circ = 4.472 \text{ k}\Omega \angle -26.57^\circ$$

$$(CDR) \quad I' = \frac{Z'I}{Z' + Z_3} = \frac{(4.472 \text{ k}\Omega \angle -26.57^\circ)(5 \text{ mA} \angle 0^\circ)}{4 \text{ k}\Omega - j2 \text{ k}\Omega + j5 \text{ k}\Omega} = \frac{22.36 \text{ mA} \angle -26.57^\circ}{5 \angle 36.87^\circ}$$
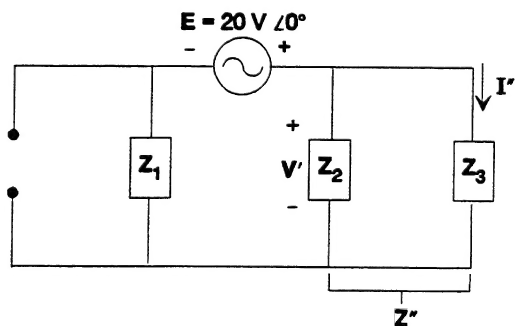
$$= 4.472 \text{ mA} \angle -63.44^\circ$$



$$(VDR) \quad V' = \frac{Z''E}{Z'' + Z_1} = \frac{(7.071 \text{ k}\Omega \angle 45^\circ)(20 \text{ V} \angle 0^\circ)}{(5 \text{ k}\Omega + j5 \text{ k}\Omega) + (10 \text{ k}\Omega)} = \frac{141.42 \text{ V} \angle 45^\circ}{15.81 \angle 18.435^\circ}$$


$$= 8.945 \text{ V} \angle 26.565^\circ$$

$$I'' = \frac{V'}{Z_3} = \frac{8.945 \text{ V} \angle 26.565^\circ}{5 \text{ k}\Omega \angle 90^\circ} = 1.789 \text{ mA} \angle -63.435^\circ = 0.8 \text{ mA} - j1.6 \text{ mA}$$

$$I = I' + I'' = (2 \text{ mA} - j4 \text{ mA}) + (0.8 \text{ mA} - j1.6 \text{ mA}) = 2.8 \text{ mA} - j5.6 \text{ mA}$$

$$= 6.261 \text{ mA} \angle -63.43^\circ$$


7.

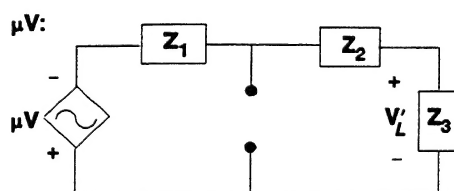

$$\begin{aligned} Z_1 &= 5 \text{ k}\Omega \angle 0^\circ, Z_2 = 1 \text{ k}\Omega \angle -90^\circ \\ Z_3 &= 4 \text{ k}\Omega \angle 0^\circ \\ V &= 2 \text{ V} \angle 0^\circ, \mu = 20 \end{aligned}$$

$$V'_L = \frac{-Z_3(\mu V)}{Z_1 + Z_2 + Z_3} = \frac{-(4 \text{ k}\Omega \angle 0^\circ)(20)(2 \text{ V} \angle 0^\circ)}{5 \text{ k}\Omega - j1 \text{ k}\Omega + 4 \text{ k}\Omega} = -17.67 \text{ V} \angle 6.34^\circ$$


I:

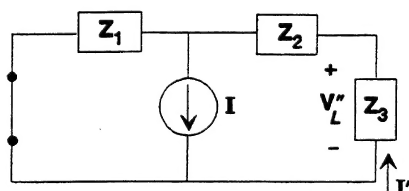

$$\begin{aligned} \text{CDR: } I' &= \frac{Z_1 I}{Z_1 + Z_2 + Z_3} \\ &= \frac{(5 \text{ k}\Omega \angle 0^\circ)(2 \text{ mA} \angle 0^\circ)}{9.056 \text{ k}\Omega \angle -6.34^\circ} \\ &= 1.104 \text{ mA} \angle 6.34^\circ \end{aligned}$$

$$\begin{aligned} V''_L &= -I'Z_3 = -(1.104 \text{ mA} \angle 6.34^\circ)(4 \text{ k}\Omega \angle 0^\circ) = -4.416 \text{ V} \angle 6.34^\circ \\ V_L &= V'_L + V''_L = -17.67 \text{ V} \angle 6.34^\circ - 4.416 \text{ V} \angle 6.34^\circ = -22.09 \text{ V} \angle 6.34^\circ \end{aligned}$$

9.

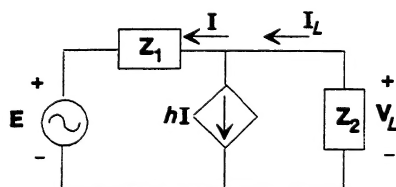

$$\begin{aligned} Z_1 &= 2 \text{ k}\Omega \angle 0^\circ, Z_2 = 2 \text{ k}\Omega \angle 0^\circ \\ V_L &= -I_L Z_2 \\ I_L &= hI + I = (h + 1)I \\ V_L &= -(h + 1)IZ_2 \\ \text{and by KVL: } V_L &= IZ_1 + E \\ \text{so that } I &= \frac{V_L - E}{Z_1} \end{aligned}$$


$$V_L = -(h + 1)IZ_2 = -(h + 1) \left[\frac{V_L - E}{Z_1} \right] Z_2$$

Subst. for Z_1, Z_2

$$V_L = -(h + 1)(V_L - E)$$

$$V_L(2 + h) = E(h + 1)$$

$$V_L = \frac{(h + 1)}{(h + 2)} E = \frac{51}{52} (20 \text{ V} \angle 53^\circ) = 19.62 \text{ V} \angle 53^\circ$$

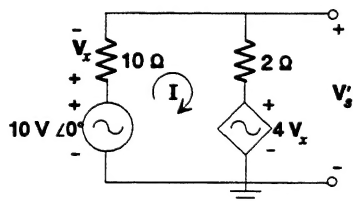11. E_1 :

$$10 \text{ V} \angle 0^\circ - I 10 \Omega - I 2 \Omega - 4 V_x = 0$$


with $V_x = I 10 \Omega$

Solving for I:

$$I = \frac{10 \text{ V} \angle 0^\circ}{52 \Omega} = 192.31 \text{ mA} \angle 0^\circ$$

$$V'_s = 10 \text{ V} \angle 0^\circ - I(10 \Omega) = 10 \text{ V} - (192.31 \text{ mA} \angle 0^\circ)(10 \Omega \angle 0^\circ) = 8.08 \text{ V} \angle 0^\circ$$

I:

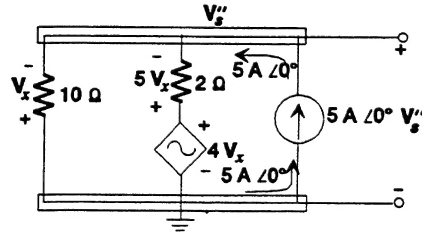


$$\begin{aligned}\Sigma I_i &= \Sigma I_o \\ 5 \text{ A } \angle 0^\circ + \frac{V_x}{10 \Omega} + \frac{5 V_x}{2 \Omega} &= 0 \\ 5 \text{ A} + 0.1 V_x + 2.5 V_x &= 0 \\ 2.6 V_x &= -5 \text{ A} \\ V_x &= -\frac{5}{2.6} \text{ V} = -1.923 \text{ V}\end{aligned}$$

$$V_s'' = -V_x = -(-1.923 \text{ V}) = 1.923 \text{ V } \angle 0^\circ$$


$$V_s = V_s' + V_s'' = 8.08 \text{ V } \angle 0^\circ + 1.923 \text{ V } \angle 0^\circ = 10 \text{ V } \angle 0^\circ$$

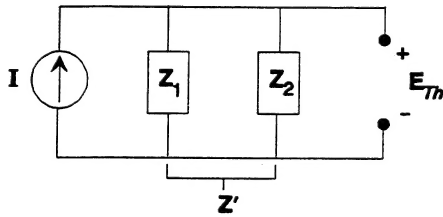13. a. From #27. $Z_{Th} = Z_1 \parallel Z_2$
 $Z_{Th} = Z_N = 21.312 \Omega \angle 32.196^\circ$



$$\begin{aligned}E_{Th} &= IZ' = IZ_{Th} \\ &= (0.1 \text{ A } \angle 0^\circ)(21.312 \Omega \angle 32.196^\circ) \\ &= 2.131 \text{ V } \angle 32.196^\circ\end{aligned}$$

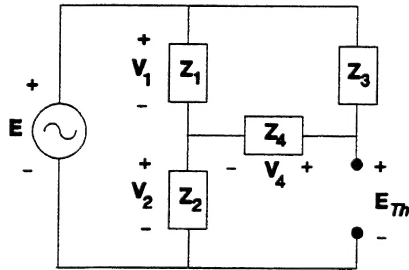- b. From #27. $Z_{Th} = Z_N = 6.813 \Omega \angle -54.228^\circ = 3.983 \Omega - j5.528 \Omega$



$$Z_1 = 2 \Omega \angle 0^\circ, Z_3 = 8 \Omega \angle -90^\circ$$

$$Z_2 = 4 \Omega \angle 90^\circ, Z_4 = 10 \Omega \angle 0^\circ$$

$$E = 50 \text{ V } \angle 0^\circ$$

$$E_{Th} = V_2 + V_4$$


$$\begin{aligned}V_2 &= \frac{Z_2 E}{Z_2 + Z_1 \parallel (Z_3 + Z_4)} \\ &= \frac{(4 \Omega \angle 90^\circ)(50 \text{ V } \angle 0^\circ)}{+j4 \Omega + 2 \Omega \angle 0^\circ \parallel (10 \Omega - j8 \Omega)} \\ &= 47.248 \text{ V } \angle 24.7^\circ\end{aligned}$$

$$V_1 = E - V_2 = 50 \text{ V } \angle 0^\circ - 47.248 \text{ V } \angle 24.7^\circ = 20.972 \text{ V } \angle -70.285^\circ$$


$$V_4 = \frac{Z_4 V_1}{Z_4 + Z_3} = \frac{(10 \Omega \angle 0^\circ)(20.972 \text{ V } \angle -70.285^\circ)}{10 \Omega - j8 \Omega} = 16.377 \text{ V } \angle -31.625^\circ$$

$$\begin{aligned}E_{Th} &= V_2 + V_4 = 47.248 \text{ V } \angle 24.7^\circ + 16.377 \text{ V } \angle -31.625^\circ \\ &= (42.925 \text{ V} + j19.743 \text{ V}) + (13.945 \text{ V} - j8.587 \text{ V}) \\ &= 56.870 \text{ V} + j11.156 \text{ V} = 57.954 \text{ V } \angle 11.099^\circ\end{aligned}$$

15. a.

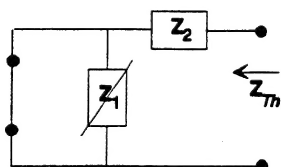

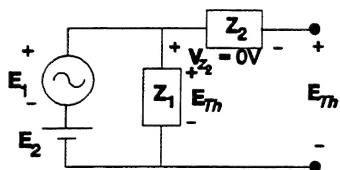
$$\begin{aligned} Z_1 &= 6 \Omega - j2 \Omega = 6.325 \Omega \angle -18.435^\circ \\ Z_2 &= 4 \Omega \angle 90^\circ \\ Z_{Th} &= Z_2 = 4 \Omega \angle 90^\circ \end{aligned}$$



By inspection:


$$\begin{aligned} E_{Th} &= E_2 + E_1 \\ &= 4 \text{ V}_{DC} + 10 \text{ V}_{AC} \angle 0^\circ \end{aligned}$$

b.

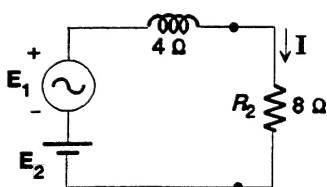

$$\begin{aligned} I &= \frac{E_2}{R_2} + \frac{E_1}{R_2 + jX_L} \\ &= \frac{4 \text{ V}}{8 \Omega} + \frac{10 \text{ V} \angle 0^\circ}{8 \Omega + j4 \Omega} \\ &= 0.5 \text{ A} + \frac{10 \text{ V} \angle 0^\circ}{8.944 \Omega \angle 26.565^\circ} \\ &= 0.5 \text{ A} + 1.118 \text{ A} \angle -26.565^\circ \\ &\quad \text{(dc)} \quad \quad \quad \text{(ac)} \end{aligned}$$

17. a. Z_{Th} :

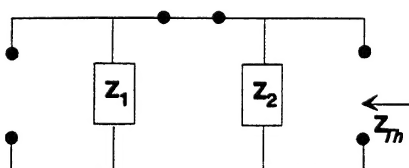


$$\begin{aligned} Z_1 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 5 \text{ k}\Omega - j5 \text{ k}\Omega \\ &= 7.071 \text{ k}\Omega \angle -45^\circ \end{aligned}$$

$$Z_{Th} = Z_1 \parallel Z_2 = (10 \text{ k}\Omega \angle 0^\circ) \parallel (7.071 \text{ k}\Omega \angle -45^\circ) = 4.472 \text{ k}\Omega \angle -26.565^\circ$$

Source conversion:

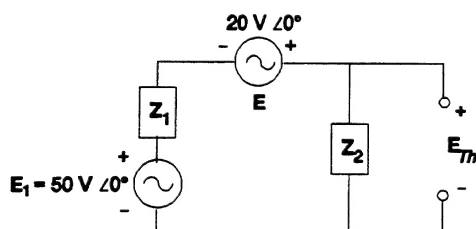
$$E_1 = (I \angle \theta)(R_1 \angle 0^\circ) = (5 \text{ mA} \angle 0^\circ)(10 \text{ k}\Omega \angle 0^\circ) = 50 \text{ V} \angle 0^\circ$$



$$\begin{aligned} E_{Th} &= \frac{Z_2(E + E_1)}{Z_2 + Z_1} \\ &= \frac{(7.071 \text{ k}\Omega \angle -45^\circ)(20 \text{ V} \angle 0^\circ + 50 \text{ V} \angle 0^\circ)}{(5 \text{ k}\Omega - j5 \text{ k}\Omega) + (10 \text{ k}\Omega)} \\ &= \frac{(7.071 \text{ k}\Omega \angle -45^\circ)(70 \text{ V} \angle 0^\circ)}{(15 \text{ k}\Omega - j5 \text{ k}\Omega)} \\ &= \frac{494.97 \text{ V} \angle -45^\circ}{15.811 \angle -18.435^\circ} \\ &= 31.31 \text{ V} \angle -26.565^\circ \end{aligned}$$


$$\begin{aligned} \text{b. } I &= \frac{E_{Th}}{Z_{Th} + Z_L} = \frac{31.31 \text{ V} \angle -26.565^\circ}{4.472 \text{ k}\Omega \angle -26.565^\circ + 5 \text{ k}\Omega \angle 90^\circ} \\ &= \frac{31.31 \text{ V} \angle -26.565^\circ}{4 \text{ k}\Omega - j2 \text{ k}\Omega + j5 \text{ k}\Omega} = \frac{31.31 \text{ V} \angle -26.565^\circ}{4 \text{ k}\Omega + j3 \text{ k}\Omega} \\ &= \frac{31.31 \text{ V} \angle -26.565^\circ}{5 \text{ k}\Omega \angle 36.87^\circ} = 6.26 \text{ mA} \angle 63.435^\circ \end{aligned}$$

19. Z_{Th} :

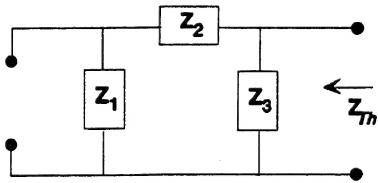

$$\begin{aligned} Z_1 &= 40 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 0.2 \text{ k}\Omega \angle -90^\circ \\ Z_3 &= 5 \text{ k}\Omega \angle 0^\circ \end{aligned}$$

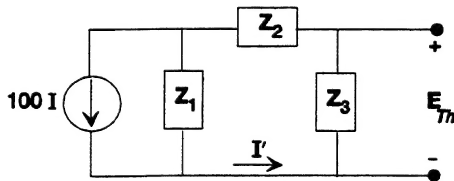
$$Z_{Th} = Z_3 \parallel (Z_1 + Z_2) = 5 \text{ k}\Omega \angle 0^\circ \parallel (40 \text{ k}\Omega - j0.2 \text{ k}\Omega) = 4.44 \text{ k}\Omega \angle -0.031^\circ$$



$$\begin{aligned} I' &= \frac{Z_1(100 \text{ I})}{Z_1 + Z_2 + Z_3} \\ &= \frac{(40 \text{ k}\Omega \angle 0^\circ)(100 \text{ I})}{45 \text{ k}\Omega \angle -0.255^\circ} \\ &= 88.89 \text{ I} \angle 0.255^\circ \end{aligned}$$


$$E_{Th} = -I'Z_3 = -(88.89 \text{ I} \angle 0.255^\circ)(5 \text{ k}\Omega \angle 0^\circ) = -444.45 \times 10^3 \text{ I} \angle 0.255^\circ$$

21. Z_{Th} :

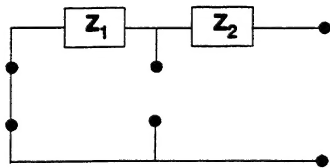


$$\begin{aligned} Z_1 &= 5 \text{ k}\Omega \angle 0^\circ & Z_2 &= -j1 \text{ k}\Omega \\ \leftarrow Z_{Th} &= Z_1 + Z_2 = 5 \text{ k}\Omega - j1 \text{ k}\Omega \\ &= 5.099 \text{ k}\Omega \angle -11.31^\circ \end{aligned}$$

E_{Th} :

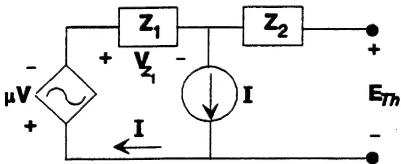


$$\begin{aligned} E_{Th} &= -[\mu V + V_{Z_1}] \\ &= -\mu V - IZ_1 \\ &= -(20)(2 \text{ V} \angle 0^\circ) - (2 \text{ mA} \angle 0^\circ)(5 \text{ k}\Omega \angle 0^\circ) \\ &= -50 \text{ V} \angle 0^\circ \end{aligned}$$

23. E_{Th} : (E_{oc})

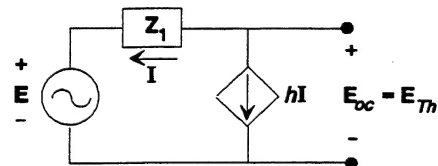

$$\begin{aligned} hI &= -I & Z_1 &= 2 \text{ k}\Omega \angle 0^\circ \\ \therefore I &= 0 \\ \text{and } hI &= 0 \\ \text{with } E_{oc} &= E_{Th} = E = 20 \text{ V} \angle 53^\circ \end{aligned}$$


I_{sc} :

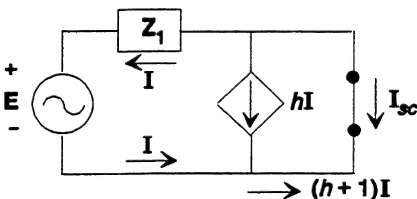

$$\begin{aligned} I_{sc} &= -(h + 1)I \\ &= -(h + 1)(10 \text{ mA} \angle 53^\circ) \\ &= -510 \text{ mA} \angle 53^\circ \end{aligned}$$

$$Z_{Th} = \frac{E_{oc}}{I_{sc}} = \frac{20 \text{ V} \angle 53^\circ}{-510 \text{ mA} \angle 53^\circ} = -39.215 \Omega \angle 0^\circ$$

25. E_{oc} :
(E_{Th})

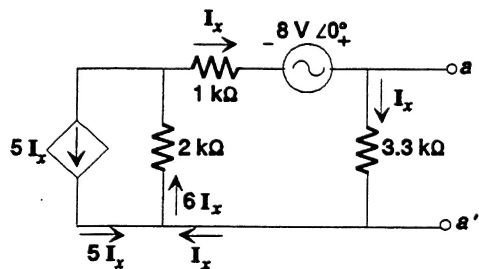


$$\text{KVL: } -6 I_x(2 \text{ k}\Omega) - I_x(1 \text{ k}\Omega) + 8 \text{ V } \angle 0^\circ - I_x(3.3 \text{ k}\Omega) = 0$$

$$I_x = \frac{8 \text{ V } \angle 0^\circ}{16.3 \text{ k}\Omega} = 0.491 \text{ mA } \angle 0^\circ$$


$$E_{oc} = E_{Th} = I_x(3.3 \text{ k}\Omega) = 1.62 \text{ V } \angle 0^\circ$$

I_{sc} :

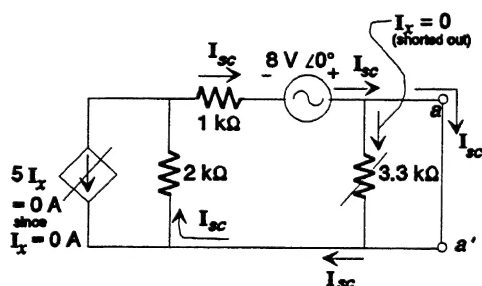


$$I_{sc} = \frac{8 \text{ V}}{3 \text{ k}\Omega} = 2.667 \text{ mA } \angle 0^\circ$$
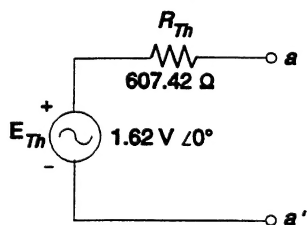
$$Z_{Th} = \frac{E_{oc}}{I_{sc}} = \frac{1.62 \text{ V } \angle 0^\circ}{2.667 \text{ mA } \angle 0^\circ} = 607.42 \text{ } \Omega$$




27. a.

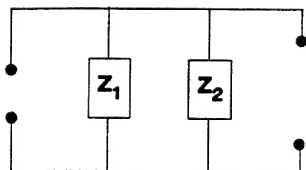

$$Z_1 = 20 \text{ } \Omega + j20 \text{ } \Omega = 28.284 \text{ } \Omega \angle 45^\circ$$

$$Z_2 = 68 \text{ } \Omega \angle 0^\circ$$

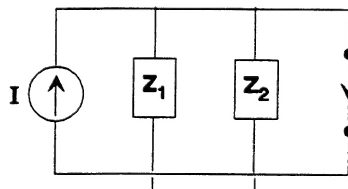
$$\begin{aligned} \leftarrow Z_N &= Z_1 \parallel Z_2 \\ &= (28.284 \text{ } \Omega \angle 45^\circ) \parallel (68 \text{ } \Omega \angle 0^\circ) \\ &= 21.312 \text{ } \Omega \angle 32.196^\circ \end{aligned}$$



Z' bypassed by short-circuit


$$I_{sc} = I = I_N = 0.1 \text{ A } \angle 0^\circ$$

b.

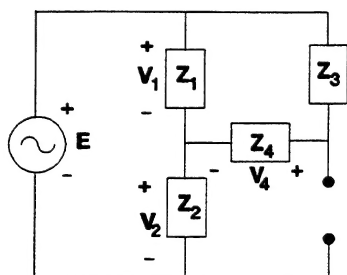

$$\begin{aligned} Z_1 &= 2 \Omega \angle 0^\circ, Z_2 = 4 \Omega \angle 90^\circ \\ Z_3 &= 8 \Omega \angle -90^\circ, Z_4 = 10 \Omega \angle 0^\circ \\ E &= 50 \text{ V} \angle 0^\circ \end{aligned}$$

Z_N :

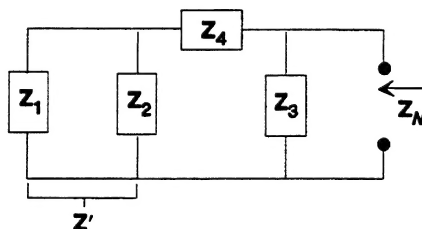


$$Z' = Z_1 \parallel Z_2 = 2 \Omega \angle 0^\circ \parallel 4 \Omega \angle 90^\circ$$

$$= 1.789 \Omega \angle 26.565^\circ = 1.6 \Omega + j0.8 \Omega$$

$$Z' + Z_4 = 1.6 \Omega + j0.8 \Omega + 10 \Omega = 11.6 \Omega + j0.8 \Omega = 11.628 \Omega \angle 3.945^\circ$$
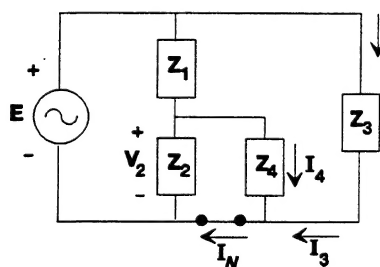
$$\begin{aligned} Z_N &= Z_3 \parallel (Z' + Z_4) = (8 \Omega \angle -90^\circ) \parallel (11.628 \Omega \angle 3.945^\circ) = 6.813 \Omega \angle -54.228^\circ \\ &= 3.983 \Omega - j5.528 \Omega \end{aligned}$$



$$I_3 = \frac{E}{Z_3} = \frac{50 \text{ V} \angle 0^\circ}{8 \Omega \angle -90^\circ} = 6.250 \text{ A} \angle 90^\circ$$


$$\begin{aligned} Z' &= Z_2 \parallel Z_4 = 4 \Omega \angle 90^\circ \parallel 10 \Omega \angle 0^\circ \\ &= 3.714 \Omega \angle 68.2^\circ \end{aligned}$$

$$\begin{aligned} V_2 &= \frac{Z'E}{Z' + Z_1} = \frac{(3.714 \Omega \angle 68.2^\circ)(50 \text{ V} \angle 0^\circ)}{1.378 \Omega + j3.448 \Omega + 2 \Omega} \\ &= \frac{185.7 \text{ V} \angle 68.2^\circ}{4.827 \angle 45.588^\circ} = 38.471 \text{ V} \angle 22.612^\circ \end{aligned}$$

$$I_4 = \frac{V_2}{Z_4} = \frac{38.471 \text{ V} \angle 22.612^\circ}{10 \Omega \angle 0^\circ} = 3.847 \text{ A} \angle 22.612^\circ$$

$$\begin{aligned} I_N &= I_3 + I_4 = 6.250 \text{ A} \angle 90^\circ + 3.847 \text{ A} \angle 22.612^\circ \\ &= +j6.25 \text{ A} + 3.551 \text{ A} + j1.479 \text{ A} = 3.551 \text{ A} + j7.729 \text{ A} \\ &= 8.506 \text{ A} \angle 65.324^\circ \end{aligned}$$


29. a. Z_N :

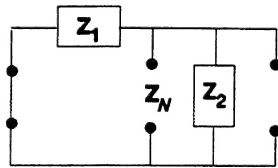

$$\begin{aligned} E &= 20 \text{ V } \angle 0^\circ, I_2 = 0.4 \text{ A } \angle 20^\circ \\ Z_1 &= 6 \Omega + j8 \Omega = 10 \Omega \angle 53.13^\circ \\ Z_2 &= 9 \Omega - j12 \Omega = 15 \Omega \angle -53.13^\circ \\ Z_N &= Z_1 \parallel Z_2 = (10 \Omega \angle 53.13^\circ) \parallel (15 \Omega \angle -53.13^\circ) \\ &= 9.66 \Omega \angle 14.93^\circ \end{aligned}$$


I_N :

(E)

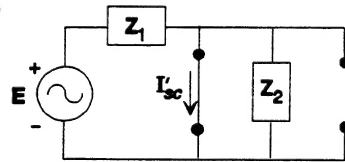

$$\begin{aligned} I'_{sc} &= E/Z_1 = 20 \text{ V } \angle 0^\circ / 10 \Omega \angle 53.13^\circ \\ &= 2 \text{ A } \angle -53.13^\circ \end{aligned}$$


(I₂)

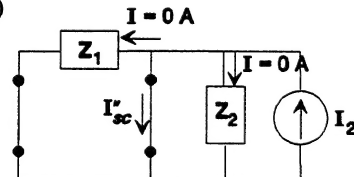

$$I''_{sc} = I_2 = 0.4 \text{ A } \angle 20^\circ$$

$$\begin{aligned} I_N &= I'_{sc} + I''_{sc} = 2 \text{ A } \angle -53.13^\circ + 0.4 \text{ A } \angle 20^\circ \\ &= 2.15 \text{ A } \angle -42.87^\circ \end{aligned}$$


b. Z_N :

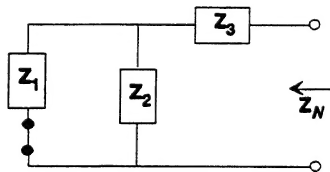

$$\begin{aligned} E_1 &= 120 \text{ V } \angle 30^\circ, Z_1 = 3 \Omega \angle 0^\circ \\ Z_2 &= 8 \Omega - j8 \Omega, Z_3 = 4 \Omega \angle 90^\circ \end{aligned}$$

$$\begin{aligned} Z_N &= Z_3 + Z_1 \parallel Z_2 \\ &= 4 \Omega \angle 90^\circ + (3 \Omega \angle 0^\circ) \parallel (8 \Omega - j8 \Omega) \\ &= 4.37 \Omega \angle 55.67^\circ = 2.465 \Omega + j3.61 \Omega \end{aligned}$$

I_N :

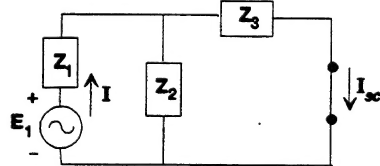


$$\begin{aligned} I &= \frac{E_1}{Z_T} = \frac{120 \text{ V } \angle 30^\circ}{Z_1 + Z_2 \parallel Z_3} \\ &= \frac{120 \text{ V } \angle 30^\circ}{3 \Omega + (8 \Omega - j8 \Omega) \parallel 4 \Omega \angle 90^\circ} \\ &= \frac{120 \text{ V } \angle 30^\circ}{6.65 \Omega \angle 46.22^\circ} \\ &= 18.05 \text{ A } \angle -16.22^\circ \end{aligned}$$

$$I_{sc} = I_N = \frac{Z_2(I)}{Z_2 + Z_3} = \frac{(8 \Omega - j8 \Omega)(18.05 \text{ A } \angle -16.22^\circ)}{8 \Omega - j8 \Omega + j4 \Omega} = 22.83 \text{ A } \angle -34.65^\circ$$


31. a. From #15 $Z_N = Z_{Th} = 9 \Omega \angle 0^\circ$

DC:

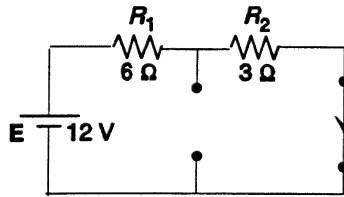

$$I'_N = \frac{E}{R_T} = \frac{12 \text{ V}}{9 \Omega} = 1.333 \text{ A}$$


AC:

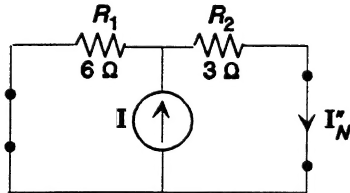

$$\begin{aligned} I''_N &= \frac{R_1 I}{R_1 + R_2} = \frac{(6 \Omega \angle 0^\circ)(4 \text{ A} \angle 0^\circ)}{9 \Omega \angle 0^\circ} \\ &= \frac{24 \text{ V} \angle 0^\circ}{9 \Omega \angle 0^\circ} = 2.667 \text{ A} \angle 0^\circ \end{aligned}$$

$$I_N = 1.333 \text{ A} + 2.667 \text{ A} \angle 0^\circ$$

- b.

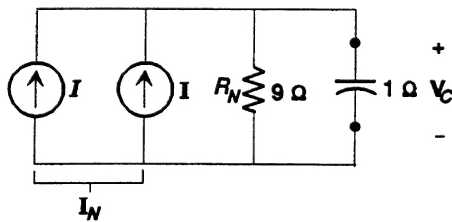


$$\begin{aligned} \text{DC: } V_C &= IR \\ &= (1.333 \text{ A})(9 \Omega) \\ &= 12 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{AC: } Z' &= 9 \Omega \angle 0^\circ \parallel 1 \Omega \angle -90^\circ \\ &= 0.994 \Omega \angle -83.66^\circ \end{aligned}$$


$$\begin{aligned} V_C &= IZ' = (2.667 \text{ A} \angle 0^\circ)(0.994 \Omega \angle -83.66^\circ) \\ &= 2.65 \text{ V} \angle -83.66^\circ \\ V_C &= 12 \text{ V} + 2.65 \text{ V} \angle -83.66^\circ \end{aligned}$$

33. Z_N :

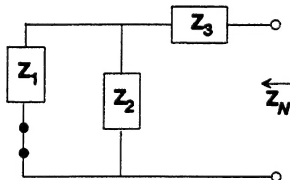

$$\begin{aligned} Z_1 &= 10 \text{ k}\Omega \angle 0^\circ, Z_2 = 10 \text{ k}\Omega \angle 0^\circ \\ Z_3 &= -j1 \text{ k}\Omega \\ Z_N &= Z_3 + Z_1 \parallel Z_2 = 5 \text{ k}\Omega - j1 \text{ k}\Omega \\ &= 5.1 \text{ k}\Omega \angle -11.31^\circ \end{aligned}$$


I_N :

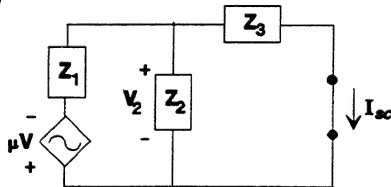

$$\begin{aligned} V_2 &= \frac{-(Z_2 \parallel Z_3)20 \text{ V}}{(Z_2 \parallel Z_3) + Z_1} \\ &= \frac{-(0.995 \text{ k}\Omega \angle -84.29^\circ)(20 \text{ V})}{0.1 \text{ k}\Omega - j0.99 \text{ k}\Omega + 10 \text{ k}\Omega} \\ V_2 &= -1.961 \text{ V} \angle -78.69^\circ \end{aligned}$$

$$I_N = I_{sc} = \frac{V_2}{Z_3} = \frac{-1.961 \text{ V} \angle -78.69^\circ}{1 \text{ k}\Omega \angle -90^\circ} = -1.961 \times 10^{-3} \text{ V} \angle 11.31^\circ$$


35. Z_N :

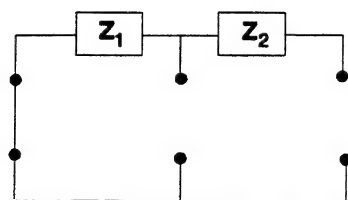

$$Z_1 = 5 \text{ k}\Omega \angle 0^\circ, Z_2 = 1 \text{ k}\Omega \angle -90^\circ$$


$$\begin{aligned} \leftarrow Z_N &= Z_1 + Z_2 = 5 \text{ k}\Omega - j1 \text{ k}\Omega \\ &= 5.1 \text{ k}\Omega \angle -11.31^\circ \end{aligned}$$

I_N : (μV)

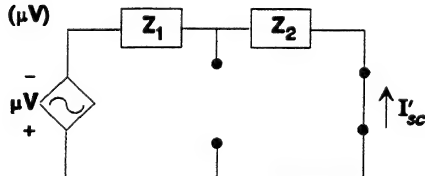

$$\begin{aligned} I'_{sc} &= \frac{\mu\text{V}}{Z_1 + Z_2} = \frac{(20)(2 \text{ V} \angle 0^\circ)}{5.1 \text{ k}\Omega \angle -11.31^\circ} \\ &= 7.843 \text{ mA} \angle 11.31^\circ \end{aligned}$$


(Ω)

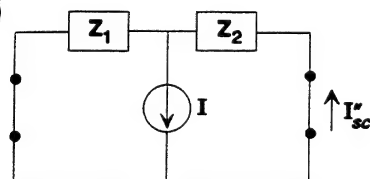

$$\begin{aligned} I''_{sc} &= \frac{Z_1(I)}{Z_1 + Z_2} \\ &= \frac{(5 \text{ k}\Omega \angle 0^\circ)(2 \text{ mA} \angle 0^\circ)}{5.1 \text{ k}\Omega \angle -11.31^\circ} \\ &= 1.96 \text{ mA} \angle 11.31^\circ \end{aligned}$$

$$\begin{aligned} I_N &= I'_{sc} + I''_{sc} = 7.843 \text{ mA} \angle 11.31^\circ + 1.96 \text{ mA} \angle 11.31^\circ \\ &= 9.81 \text{ mA} \angle 11.31^\circ \end{aligned}$$

37.

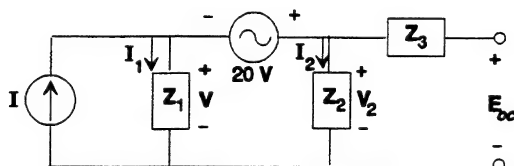

$$Z_1 = 1 \text{ k}\Omega \angle 0^\circ$$

$$Z_2 = 3 \text{ k}\Omega \angle 0^\circ$$

$$Z_3 = 4 \text{ k}\Omega \angle 0^\circ$$

$$V_2 = 21 \text{ V} = E_{oc} \Rightarrow V = \frac{E_{oc}}{21}$$


$$I = I_1 + I_2, I_1 = \frac{V}{Z_1} = \frac{E_{oc}}{21 Z_1}$$

$$I_2 = \frac{E_{oc}}{Z_2}, I = I_1 + I_2 = \frac{E_{oc}}{21 Z_1} + \frac{E_{oc}}{Z_2} = E_{oc} \left[\frac{1}{21 Z_1} + \frac{1}{Z_2} \right]$$

$$I = E_{oc} \left[\frac{Z_2 + 21 Z_1}{21 Z_1 Z_2} \right]$$

$$\text{and } E_{oc} = \frac{21 Z_1 Z_2 I}{Z_2 + 21 Z_1} = \frac{(21)(1 \text{ k}\Omega \angle 0^\circ)(3 \text{ k}\Omega \angle 0^\circ)(2 \text{ mA} \angle 0^\circ)}{3 \text{ k}\Omega + 21(1 \text{ k}\Omega \angle 0^\circ)}$$
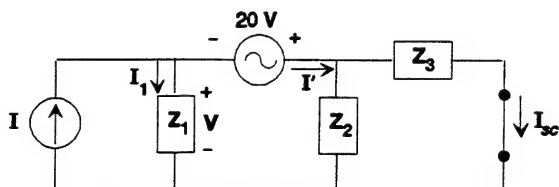
$$E_{Th} = E_{oc} = 5.25 \text{ V} \angle 0^\circ$$



$$I_{sc} = \frac{V_3}{Z_3} = \frac{21 \text{ V}}{Z_3} \Rightarrow V = \frac{Z_3}{21} I_{sc}$$

$$V = I_1 Z_1$$

$$I = I_1 + I'$$

$$I_{sc} = \frac{Z_2 I'}{Z_2 + Z_3} \Rightarrow I' = \left[\frac{Z_2 + Z_3}{Z_2} \right] I_{sc}$$


$$I = I_1 + I' = \frac{V}{Z_1} + \left[\frac{Z_2 + Z_3}{Z_2} \right] I_{sc} = \left[\frac{Z_3}{21 Z_1} + \frac{Z_2 + Z_3}{Z_2} \right] I_{sc}$$

$$I_{sc} = \frac{I}{\frac{Z_3}{21 Z_1} + \frac{Z_3 + Z_2}{Z_2}} = \frac{2 \text{ mA } \angle 0^\circ}{\frac{4 \text{ k}\Omega}{21 \text{ k}\Omega} + \frac{7 \text{ k}\Omega}{3 \text{ k}\Omega}} = 0.792 \text{ mA } \angle 0^\circ$$

$$\therefore I_N = 0.792 \text{ mA } \angle 0^\circ$$

$$Z_N = \frac{E_{oc}}{I_{sc}} = \frac{5.25 \text{ V } \angle 0^\circ}{0.792 \text{ mA } \angle 0^\circ} = 6.63 \text{ k}\Omega \angle 0^\circ$$

39. a.

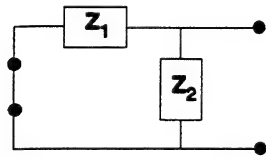


$$Z_1 = 3 \Omega + j4 \Omega, Z_2 = -j6 \Omega$$

$$\leftarrow Z_{Th} = Z_1 \parallel Z_2$$

$$= 5 \Omega \angle 53.13^\circ \parallel 6 \Omega \angle -90^\circ$$

$$= 8.32 \Omega \angle -3.18^\circ$$
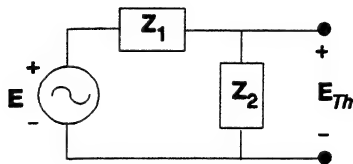
$$Z_L = 8.32 \Omega \angle 3.18^\circ = 8.31 \Omega - j0.462 \Omega$$




$$E_{Th} = \frac{Z_2 E}{Z_2 + Z_1}$$

$$= \frac{(6 \Omega \angle -90^\circ)(120 \text{ V } \angle 0^\circ)}{3.61 \Omega \angle -33.69^\circ}$$

$$= 199.45 \text{ V } \angle -56.31^\circ$$

$$P_{max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(199.45 \text{ V})^2}{4(8.31 \Omega)} = 1198.2 \text{ W}$$

b.

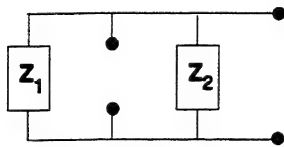

$$Z_1 = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ$$

$$Z_2 = 2 \Omega \angle 0^\circ$$

$$\leftarrow Z_N = Z_{Th} = Z_1 \parallel Z_2$$

$$= 5 \Omega \angle 53.13^\circ \parallel 2 \Omega \angle 0^\circ$$

$$= \frac{10 \Omega \angle 53.13^\circ}{2 + 3 + j4}$$

$$= \frac{10 \Omega \angle 53.13^\circ}{5 + j4}$$


$$= \frac{10 \Omega \angle 53.13^\circ}{6.403 \angle 38.66^\circ}$$

$$= 1.562 \Omega \angle 14.47^\circ$$

$$Z_{Th} = 1.562 \Omega \angle 14.47^\circ$$

$$= 1.512 \Omega + j0.39 \Omega$$

$$Z_L = 1.512 \Omega - j0.39 \Omega$$

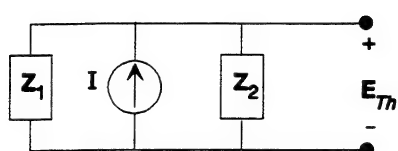


$$E_{Th} = I(Z_1 \parallel Z_2)$$

$$= (2 \text{ A } \angle 30^\circ)(1.562 \Omega \angle 14.47^\circ)$$


$$= 3.124 \text{ V } \angle 44.47^\circ$$

$$P_{max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(3.124 \text{ V})^2}{4(1.512 \Omega)} = 1.614 \text{ W}$$

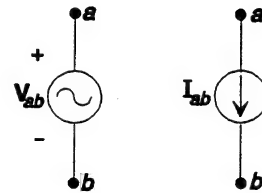41. $I = \frac{E \angle 0^\circ}{R_1 \angle 0^\circ} = \frac{1 \text{ V} \angle 0^\circ}{1 \text{ k}\Omega \angle 0^\circ} = 1 \text{ mA} \angle 0^\circ$
 $Z_{Th} = 40 \text{ k}\Omega \angle 0^\circ$
 $E_{Th} = (50 \text{ I})(40 \text{ k}\Omega \angle 0^\circ) = (50)(1 \text{ mA} \angle 0^\circ)(40 \text{ k}\Omega \angle 0^\circ) = 2000 \text{ V} \angle 0^\circ$
 $P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(2 \text{ kV})^2}{4(40 \text{ k}\Omega)} = 25 \text{ W}$
43. From #16, $Z_{Th} = 9 \Omega$, $E_{Th} = 12 \text{ V} + 24 \text{ V} \angle 0^\circ$
- a. $\therefore Z_L = 9 \Omega$
- b. $P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(12 \text{ V})^2}{4(9 \Omega)} + \frac{(24 \text{ V})^2}{4(9 \Omega)} = 4 \text{ W} + 16 \text{ W} = 20 \text{ W}$
or $E_{Th} = \sqrt{V_0^2 + V_{l_{\text{eff}}}^2} = 26.833 \text{ V}$
and $P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(26.833 \text{ V})^2}{4(9 \Omega)} = 20 \text{ W}$
45. a. $Z_{Th} = 2 \text{ k}\Omega \angle 0^\circ \parallel 2 \text{ k}\Omega \angle -90^\circ = 1 \text{ k}\Omega - j1 \text{ k}\Omega$
 $R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_{\text{Load}})^2}$
 $= \sqrt{(1 \text{ k}\Omega)^2 + (-1 \text{ k}\Omega + 2 \text{ k}\Omega)^2}$
 $= \sqrt{(1 \text{ k}\Omega)^2 + (1 \text{ k}\Omega)^2}$
 $= 1.414 \text{ k}\Omega$
- b. $R_{\text{av}} = (R_{Th} + R_{\text{Load}})/2 = (1 \text{ k}\Omega + 1.414 \text{ k}\Omega)/2 = 1.207 \text{ k}\Omega$
 $P_{\max} = \frac{E_{Th}^2}{4R_{\text{av}}} = \frac{(50 \text{ V})^2}{4(1.207 \text{ k}\Omega)} = 0.518 \text{ W}$
47. $I_{ab} = \frac{(4 \text{ k}\Omega \angle 0^\circ)(4 \text{ mA} \angle 0^\circ)}{4 \text{ k}\Omega + 8 \text{ k}\Omega} = 1.333 \text{ mA} \angle 0^\circ$
 $V_{ab} = (I_{ab})(8 \text{ k}\Omega \angle 0^\circ) = 10.67 \text{ V} \angle 0^\circ$



49.

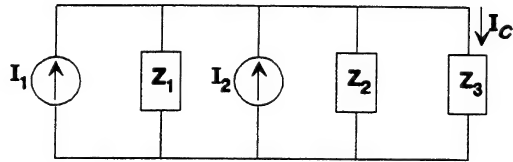

$$I_1 = \frac{100 \text{ V } \angle 0^\circ}{2 \text{ k}\Omega \angle 0^\circ} = 50 \text{ mA } \angle 0^\circ$$

$$I_2 = \frac{50 \text{ V } \angle 0^\circ}{4 \text{ k}\Omega \angle 90^\circ} = 12.5 \text{ mA } \angle -90^\circ$$

$$Z_1 = 2 \text{ k}\Omega \angle 0^\circ$$

$$Z_2 = 4 \text{ k}\Omega \angle 90^\circ$$

$$Z_3 = 4 \text{ k}\Omega \angle -90^\circ$$


$$I_T = I_1 - I_2 = (50 \text{ mA } \angle 0^\circ - 12.5 \text{ mA } \angle -90^\circ) = 50 \text{ mA} + j12.5 \text{ mA} \\ = 51.54 \text{ mA } \angle 14.04^\circ$$

$$Z' = Z_1 \parallel Z_2 = (2 \text{ k}\Omega \angle 0^\circ) \parallel (4 \text{ k}\Omega \angle 90^\circ) = 1.79 \text{ k}\Omega \angle 26.57^\circ$$

$$I_C = \frac{Z' I_T}{Z' + Z_3} = \frac{(1.79 \text{ k}\Omega \angle 26.57^\circ)(51.54 \text{ mA } \angle 14.04^\circ)}{1.6 \text{ k}\Omega + j0.8 \text{ k}\Omega - j4 \text{ k}\Omega} \\ = 25.77 \text{ mA } \angle 104.04^\circ$$

CHAPTER 18 (Even)

2. a. E_1 :

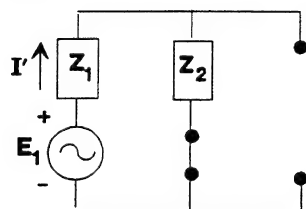


$$E_1 = 20 \text{ V } \angle 0^\circ, \quad Z_1 = 4 \Omega + j3 \Omega = 5 \Omega \angle 36.87^\circ$$

$$Z_2 = 1 \Omega \angle 0^\circ$$

$$I' = \frac{E_1}{Z_1 + Z_2} = \frac{20 \text{ V } \angle 0^\circ}{4 \Omega + j3 \Omega + 1 \Omega}$$

$$= 3.43 \text{ A } \angle -30.96^\circ$$


E_2 :

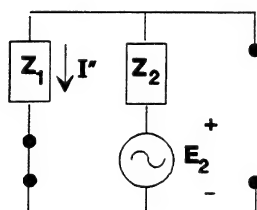

$$I'' = \frac{E_2}{Z_1 + Z_2} = \frac{120 \text{ V } \angle 0^\circ}{5.83 \Omega \angle 30.96^\circ}$$

$$= 20.58 \text{ A } \angle -30.96^\circ$$

I :

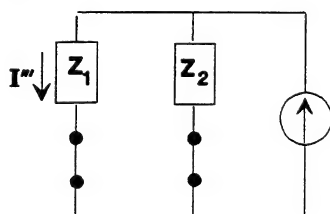

$$I''' = \frac{Z_2 I}{Z_2 + Z_1} = \frac{(1 \Omega \angle 0^\circ)(0.5 \text{ A } \angle 60^\circ)}{5.83 \Omega \angle 30.96^\circ}$$


$$= 0.0858 \text{ A } \angle 29.04^\circ$$

$$\uparrow I_L = I' - I'' - I'''$$

$$= (3.43 \text{ A } \angle -30.96^\circ) - (20.58 \text{ A } \angle -30.96^\circ) - (0.0858 \text{ A } \angle 29.04^\circ)$$

$$= 17.20 \text{ A } \angle 149.30^\circ \text{ or } 17.20 \text{ A } \angle -30.70^\circ \downarrow$$

b. E :

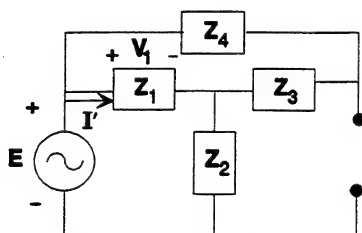

$$Z_1 = 3 \Omega \angle 90^\circ, \quad Z_2 = 7 \Omega \angle -90^\circ$$

$$E = 10 \text{ V } \angle 90^\circ$$

$$Z_3 = 6 \Omega \angle -90^\circ, \quad Z_4 = 4 \Omega \angle 0^\circ$$

$$Z' = Z_1 \parallel (Z_3 + Z_4)$$


$$= 3 \Omega \angle 90^\circ \parallel (4 \Omega - j6 \Omega)$$

$$= 3 \Omega \angle 90^\circ \parallel 7.21 \Omega \angle -56.31^\circ$$

$$= 4.33 \Omega \angle 70.56^\circ$$

$$\begin{aligned}
 V_1 &= \frac{Z'E}{Z' + Z_2} \\
 &= \frac{(4.33 \Omega \angle 70.56^\circ)(10 \text{ V} \angle 90^\circ)}{(1.44 \Omega + j4.08 \Omega) - j7\Omega} \\
 &= \frac{43.3 \text{ V} \angle 160.56^\circ}{3.26 \angle -63.75^\circ} = 13.28 \text{ V} \angle 224.31^\circ \\
 I' &= \frac{V_1}{Z_1} = \frac{13.28 \text{ V} \angle 224.31^\circ}{3 \Omega \angle 90^\circ} \\
 &= 4.43 \text{ A} \angle 134.31^\circ
 \end{aligned}$$

I:

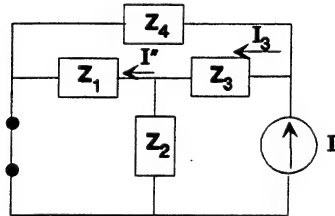

$$\begin{aligned}
 Z'' &= Z_3 + Z_1 \parallel Z_2 \\
 &= -j6 \Omega + 3 \Omega \angle 90^\circ \parallel 7 \Omega \angle -90^\circ \\
 &= -j6 \Omega + 5.25 \Omega \angle 90^\circ \\
 &= -j6 \Omega + j5.25 \Omega \\
 &= -j0.75 \Omega = 0.75 \Omega \angle -90^\circ
 \end{aligned}$$


CDR:

$$\begin{aligned}
 I_3 &= \frac{Z_4 I}{Z_4 + Z''} = \frac{(4 \Omega \angle 0^\circ)(0.6 \text{ A} \angle 120^\circ)}{4 \Omega - j0.75 \Omega} = \frac{2.4 \text{ A} \angle 120^\circ}{4.07 \angle -10.62^\circ} \\
 &= 0.59 \text{ A} \angle 130.62^\circ
 \end{aligned}$$


$$\begin{aligned}
 I'' &= \frac{Z_2 I_3}{Z_2 + Z_1} = \frac{(7 \Omega \angle -90^\circ)(0.59 \text{ A} \angle 130.62^\circ)}{-j7 \Omega + j3 \Omega} = \frac{4.13 \text{ A} \angle 40.62^\circ}{4 \angle -90^\circ} \\
 &= 1.03 \text{ A} \angle 130.62^\circ
 \end{aligned}$$

$$\begin{aligned}
 I_L &= I' - I'' \text{ (direction of } I') \\
 &= 4.43 \text{ A} \angle 134.31^\circ - 1.03 \text{ A} \angle 130.62^\circ \\
 &= (-3.09 \text{ A} + j3.17 \text{ A}) - (-0.67 \text{ A} + j0.78 \text{ A}) = -2.42 \text{ A} + j2.39 \text{ A} \\
 &= 3.40 \text{ A} \angle 135.36^\circ
 \end{aligned}$$

4. DC:

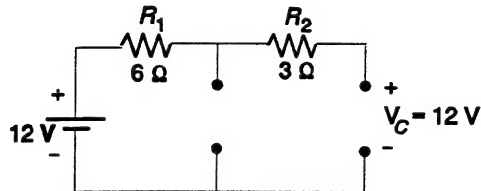


AC:

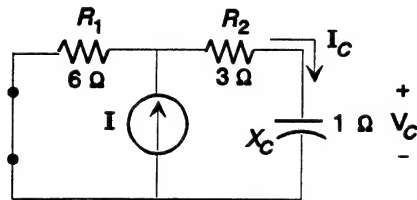

$$\begin{aligned}
 I_C &= \frac{(6 \Omega \angle 0^\circ)(I)}{6 \Omega + 3 \Omega - j1 \Omega} \\
 &= \frac{(6 \Omega \angle 0^\circ)(4 \text{ A} \angle 0^\circ)}{9 \Omega - j1 \Omega} \\
 &= \frac{24 \text{ A} \angle 0^\circ}{9.055 \angle -6.34^\circ} \\
 &= 2.65 \text{ A} \angle 6.34^\circ
 \end{aligned}$$


$$\begin{aligned}
 V_C &= I_C X_C = (2.65 \text{ A} \angle 6.34^\circ)(1 \Omega \angle -90^\circ) = 2.65 \text{ V} \angle -83.66^\circ \\
 &= 12 \text{ V} + 2.65 \text{ V} \angle -83.66^\circ \\
 v_C &= 12 \text{ V} + 3.747 \sin(\omega t - 83.66^\circ)
 \end{aligned}$$

6.

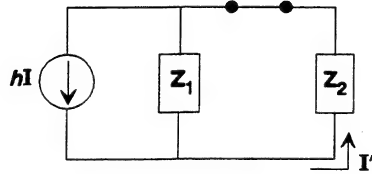

$$\begin{aligned} Z_1 &= 20 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 10 \text{ k}\Omega \angle 90^\circ \\ I &= 2 \text{ mA} \angle 0^\circ \\ E &= 10 \text{ V} \angle 0^\circ \end{aligned}$$

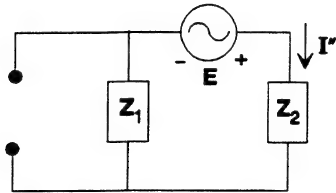
$$I' = \frac{Z_1(hI)}{Z_1 + Z_2} = \frac{(20 \text{ k}\Omega \angle 0^\circ)(100)(2 \text{ mA} \angle 0^\circ)}{20 \text{ k}\Omega + j10 \text{ k}\Omega} = 0.179 \text{ A} \angle -26.57^\circ$$



$$\begin{aligned} I'' &= \frac{E}{Z_1 + Z_2} = \frac{10 \text{ V} \angle 0^\circ}{22.36 \text{ k}\Omega \angle 26.57^\circ} \\ &= 0.447 \text{ mA} \angle -26.57^\circ \end{aligned}$$


$$\begin{aligned} I_L &= I' - I'' \text{ (direction of } I') \\ &= 179 \text{ mA} \angle -26.57^\circ - 0.447 \text{ mA} \angle -26.57^\circ \\ &= 178.55 \text{ mA} \angle -26.57^\circ \end{aligned}$$

8.

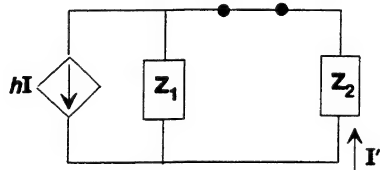

$$\begin{aligned} Z_1 &= 20 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 5 \text{ k}\Omega + j5 \text{ k}\Omega \end{aligned}$$

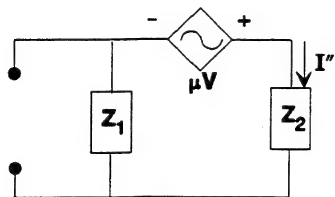
$$I' = \frac{Z_1(hI)}{Z_1 + Z_2} = \frac{(20 \text{ k}\Omega \angle 0^\circ)(100)(1 \text{ mA} \angle 0^\circ)}{20 \text{ k}\Omega + 5 \text{ k}\Omega + j5 \text{ k}\Omega} = 78.45 \text{ mA} \angle -11.31^\circ$$



$$\begin{aligned} I'' &= \frac{\mu V}{Z_1 + Z_2} = \frac{(20)(10 \text{ V} \angle 0^\circ)}{25.495 \text{ k}\Omega \angle 11.31^\circ} \\ &= 7.845 \text{ mA} \angle -11.31^\circ \end{aligned}$$

$$\begin{aligned} I_L &= I' - I'' \text{ (direction of } I') \\ &= 78.45 \text{ mA} \angle -11.31^\circ - 7.845 \text{ mA} \angle -11.31^\circ \\ &= 70.61 \text{ mA} \angle -11.31^\circ \end{aligned}$$

10. I_1 :

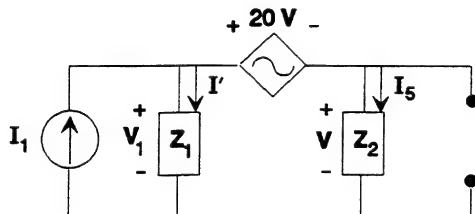

$$\begin{aligned} I_1 &= 1 \text{ mA} \angle 0^\circ \\ Z_1 &= 2 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 5 \text{ k}\Omega \angle 0^\circ \end{aligned}$$

$$\begin{aligned} \text{KVL: } V_1 - 20 \text{ V} - V &= 0 \quad I' = \frac{V_1}{Z_1} \therefore I' = \frac{21 \text{ V}}{Z_1} \text{ or } V = \frac{Z_1 I'}{21} \\ V_1 &= 21 \text{ V} \end{aligned}$$

(Even)


$$V = I_5 Z_2 = [I_1 - I'] Z_2$$

$$\frac{Z_1}{21} I' = I_1 Z_2 - I' Z_2$$

$$I' \left[\frac{Z_1}{21} + Z_2 \right] = I_1 Z_2$$

$$\text{and } I' = \frac{Z_2}{\frac{Z_1}{21} + Z_2} [I_1] = \frac{(5 \text{ k}\Omega \angle 0^\circ)(1 \text{ mA} \angle 0^\circ)}{\left[\frac{2 \text{ k}\Omega \angle 0^\circ}{21} \right] + 5 \text{ k}\Omega \angle 0^\circ} = 0.981 \text{ mA} \angle 0^\circ$$

I_2 :

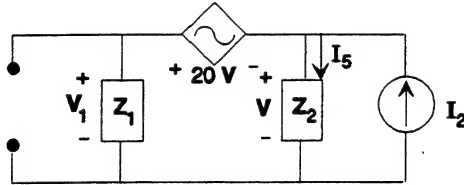

$$V_1 = 20 \text{ V} + V = 21 \text{ V}$$

$$I'' = \frac{V_1}{Z_1} = \frac{21 \text{ V}}{Z_1} \Rightarrow V = \frac{Z_1}{21} I''$$

$$I_5 = \frac{V}{Z_2} = \frac{Z_1}{21 Z_2} I''$$


$$I'' = I_2 - I_5 = I_2 - \frac{Z_1}{21 Z_2} I''$$

$$I'' \left[1 + \frac{Z_1}{21 Z_2} \right] = I_2$$

$$I'' = \frac{I_2}{1 + \frac{Z_1}{21 Z_2}} = \frac{2 \text{ mA} \angle 0^\circ}{1 + \frac{2 \text{ k}\Omega}{21(5 \text{ k}\Omega)}} = 1.963 \text{ mA} \angle 0^\circ$$

$$I = I' + I'' = 0.981 \text{ mA} \angle 0^\circ + 1.963 \text{ mA} \angle 0^\circ = 2.944 \text{ mA} \angle 0^\circ$$

12. a. Z_{Th} :

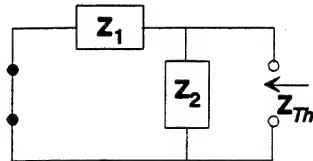


$$Z_1 = 3 \Omega \angle 0^\circ, Z_2 = 4 \Omega \angle 90^\circ$$

$$E = 100 \text{ V} \angle 0^\circ$$


$$Z_{Th} = Z_1 \parallel Z_2 = (3 \Omega \angle 0^\circ \parallel 4 \Omega \angle 90^\circ) = 2.4 \Omega \angle 36.87^\circ = 1.92 \Omega + j1.44 \Omega$$

E_{Th} :

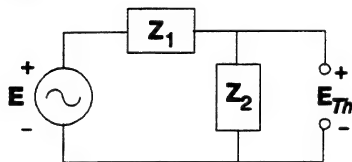


$$E_{Th} = \frac{Z_2 E}{Z_2 + Z_1} = \frac{(4 \Omega \angle 90^\circ)(100 \text{ V} \angle 0^\circ)}{5 \Omega \angle 53.13^\circ} = 80 \text{ V} \angle 36.87^\circ$$

b. Z_{Th} :

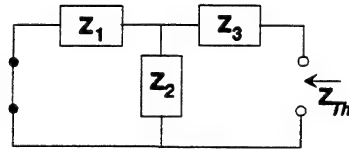


$$\begin{aligned} Z_{Th} &= Z_3 + Z_1 \parallel Z_2 \\ &= +j6 \text{ k}\Omega + (2 \text{ k}\Omega \angle 0^\circ \parallel 3 \text{ k}\Omega \angle -90^\circ) \\ &= +j6 \text{ k}\Omega + 1.664 \text{ k}\Omega \angle -33.69^\circ \\ &= +j6 \text{ k}\Omega + 1.385 \text{ k}\Omega - j0.923 \text{ k}\Omega \\ &= 1.385 \text{ k}\Omega + j5.077 \text{ k}\Omega \\ &= 5.263 \text{ k}\Omega \angle 74.741^\circ \end{aligned}$$

E_{Th} :

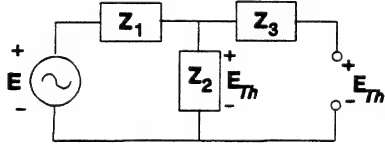

$$\begin{aligned} E_{Th} &= \frac{Z_2 E}{Z_2 + Z_1} = \frac{(3 \text{ k}\Omega \angle -90^\circ)(20 \text{ V} \angle 0^\circ)}{2 \text{ k}\Omega - j3 \text{ k}\Omega} \\ &= \frac{60 \text{ V} \angle -90^\circ}{3.606 \angle -56.31^\circ} = 16.639 \text{ V} \angle -33.69^\circ \end{aligned}$$

14. a. Z_{Th} :

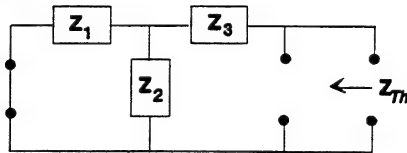


$$\begin{aligned} Z_1 &= 10 \Omega \angle 0^\circ, Z_2 = 8 \Omega \angle 90^\circ \\ Z_3 &= 8 \Omega \angle -90^\circ \end{aligned}$$

$$\begin{aligned} Z_{Th} &= Z_3 + Z_1 \parallel Z_2 \\ &= -j8 \Omega + 10 \Omega \angle 0^\circ \parallel 8 \Omega \angle 90^\circ \\ &= -j8 \Omega + 6.247 \Omega \angle 51.34^\circ \\ &= -j8 \Omega + 3.902 \Omega + j4.878 \Omega \\ &= 3.902 \Omega - j3.122 \Omega \\ &= 4.997 \Omega \angle -38.663^\circ \end{aligned}$$


E_{Th} : Superposition:

(E_1)

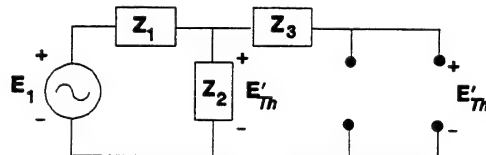

$$\begin{aligned} E'_{Th} &= \frac{(8 \Omega \angle 90^\circ)(120 \text{ V} \angle 0^\circ)}{10 \Omega + j8 \Omega} \\ &= \frac{960 \text{ V} \angle 90^\circ}{12.806 \angle 38.66^\circ} \\ &= 74.965 \text{ V} \angle 51.34^\circ \end{aligned}$$


(I)

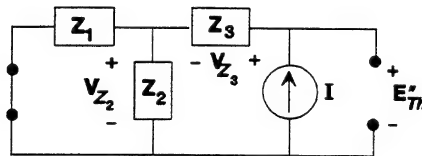

$$\begin{aligned} E''_{Th} &= V_{Z_2} + V_{Z_3} \\ &= IZ_3 + I(Z_1 \parallel Z_2) \\ &= I(Z_3 + Z_1 \parallel Z_2) \\ &= (0.5 \text{ A} \angle 60^\circ)(-j8 \Omega + 10 \Omega \angle 0^\circ \parallel 8 \Omega \angle 90^\circ) \\ &= (0.5 \text{ A} \angle 60^\circ)(-j8 \Omega + 3.902 \Omega + j4.878 \Omega) \\ &= (0.5 \text{ A} \angle 60^\circ)(3.902 \Omega - j3.122 \Omega) \\ &= (0.5 \text{ A} \angle 60^\circ)(4.997 \Omega \angle -38.663^\circ) \\ &= 2.499 \text{ V} \angle 21.337^\circ \end{aligned}$$


$$\begin{aligned}
 E_{Th} &= E'_{Th} + E''_{Th} \\
 &= 74.965 \text{ V } \angle 51.34^\circ + 2.449 \text{ V } \angle 21.337^\circ \\
 &= (46.83 \text{ V} + j58.538 \text{ V}) + (2.328 \text{ V} + j0.909 \text{ V}) \\
 &= 49.158 \text{ V} + j59.447 \text{ V} = 77.139 \text{ V } \angle 50.412^\circ
 \end{aligned}$$

b. Z_{Th} :

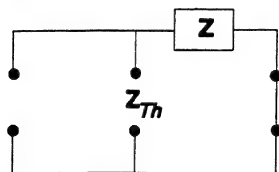


$$Z_{Th} = Z = 10 \Omega - j10 \Omega = 14.142 \Omega \angle -45^\circ$$

E_{Th} :

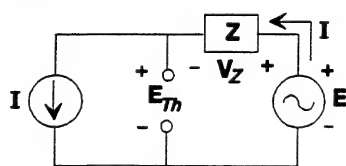


$$\begin{aligned}
 E_{Th} &= E - V_Z \\
 &= 20 \text{ V } \angle 40^\circ - IZ \\
 &= 20 \text{ V } \angle 40^\circ - (0.6 \text{ A } \angle 90^\circ)(14.142 \Omega \angle -45^\circ) \\
 &= 20 \text{ V } \angle 40^\circ - 8.485 \text{ V } \angle 45^\circ \\
 &= (15.321 \text{ V} + j12.856 \text{ V}) - (6 \text{ V} + j6 \text{ V}) \\
 &= 9.321 \text{ V} + j6.856 \text{ V} \\
 &= 11.571 \text{ V } \angle 36.336^\circ
 \end{aligned}$$

16. a. Z_{Th} :

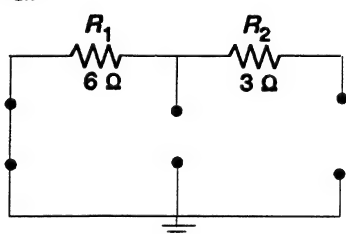


$$\leftarrow Z_{Th} = Z_{R_1} + Z_{R_2} = 6 \Omega + 3 \Omega = 9 \Omega$$

DC:

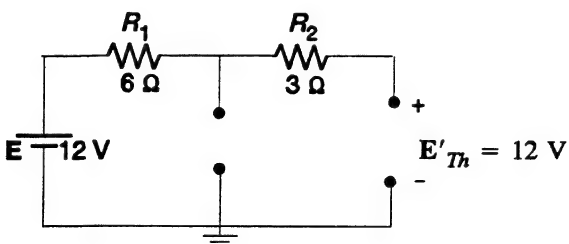

$$E'_{Th} = 12 \text{ V}$$


AC:

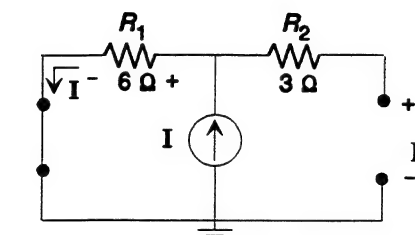

$$E''_{Th} = IZ_{R_1} = (4 \text{ A } \angle 0^\circ)(6 \Omega \angle 0^\circ) = 24 \text{ V } \angle 0^\circ$$

$$E_{Th} = 12 \text{ V (DC)} + 24 \text{ V } \angle 0^\circ \text{ (AC)}$$

b.

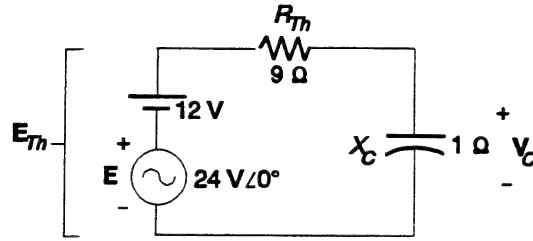


DC: $V_C = 12 \text{ V}$

$$\begin{aligned} \text{AC: } V_C &= \frac{Z_C E}{Z_C + Z_{R_{Th}}} \\ &= \frac{(1 \Omega \angle -90^\circ)(24 \text{ V} \angle 0^\circ)}{-j1 \Omega + 9 \Omega} \\ &= \frac{24 \text{ V} \angle -90^\circ}{9.055 \angle -6.34^\circ} \\ V_C &= 2.65 \text{ V} \angle -83.66^\circ \end{aligned}$$

$$\begin{aligned} v_C &= 12 \text{ V} + 2.65 \text{ V} \angle -83.66^\circ \\ &= 12 \text{ V} + 3.747 \sin(\omega t - 83.66^\circ) \end{aligned}$$

18.

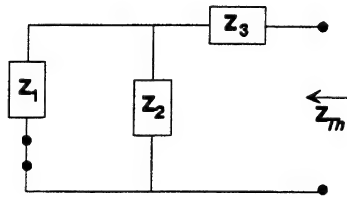


$$\begin{aligned} Z_1 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_3 &= 1 \text{ k}\Omega \angle -90^\circ \end{aligned}$$

$$Z_{Th} = Z_3 + Z_1 \parallel Z_2 = 5 \text{ k}\Omega - j1 \text{ k}\Omega \approx 5.1 \text{ k}\Omega \angle -11.31^\circ$$


$$E_{Th}: \text{ (VDR)} \quad E_{Th} = \frac{Z_2(20 \text{ V})}{Z_2 + Z_1} = \frac{(10 \text{ k}\Omega \angle 0^\circ)(20 \text{ V})}{10 \text{ k}\Omega + 10 \text{ k}\Omega} = 10 \text{ V}$$

20.

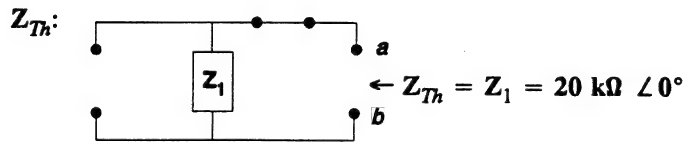


$$Z_{Th} = Z_1 = 20 \text{ k}\Omega \angle 0^\circ$$

E_{Th} :

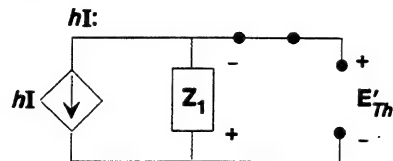

$$\begin{aligned} E'_{Th} &= -(hI)(Z_1) \\ &= -(100)(2 \text{ mA} \angle 0^\circ)(20 \text{ k}\Omega \angle 0^\circ) \\ &= -4 \text{ kV} \angle 0^\circ \end{aligned}$$


E :

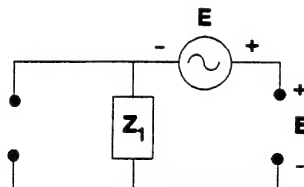

$$E'_{Th} = E = 10 \text{ V} \angle 0^\circ$$

$$\begin{aligned} E_{Th} &= E'_{Th} + E''_{Th} \\ &= -4 \text{ kV} \angle 0^\circ + 10 \text{ V} \angle 0^\circ \\ &= -3990 \text{ V} \angle 0^\circ \end{aligned}$$

22. Z_{Th} :

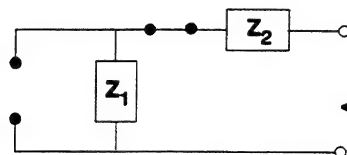


$$\begin{aligned} Z_1 &= 20 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 5 \text{ k}\Omega \angle 0^\circ \end{aligned}$$


$$Z_{Th} = Z_1 + Z_2 = 25 \text{ k}\Omega \angle 0^\circ$$

(Even)

E_{Th} :

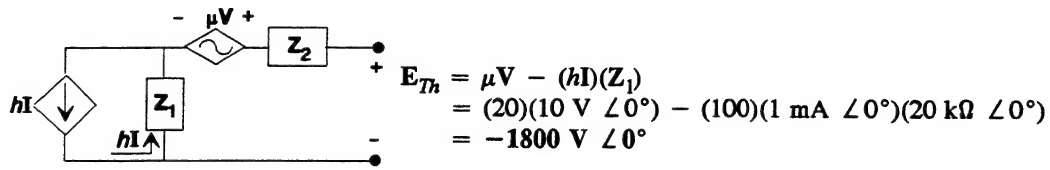

24. E_{Th} :

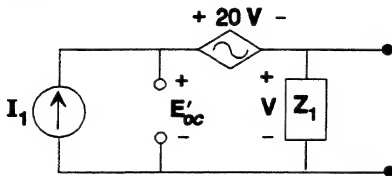


$$E'_{oc} = 21 \text{ V} \quad Z_1 = 5 \text{ k}\Omega \angle 0^\circ$$

$$V = I_1 Z_1 = (1 \text{ mA } \angle 0^\circ)(5 \text{ k}\Omega \angle 0^\circ)$$

$$= 5 \text{ V } \angle 0^\circ$$

$$E'_{oc} = E'_{Th} = 21(5 \text{ V } \angle 0^\circ)$$

$$= 105 \text{ V } \angle 0^\circ$$

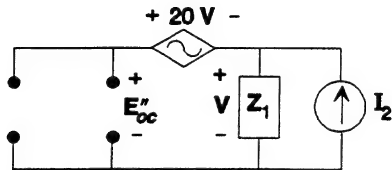


$$V = I_2 Z_1$$

$$= (2 \text{ mA } \angle 0^\circ)(5 \text{ k}\Omega \angle 0^\circ)$$


$$= 10 \text{ V } \angle 0^\circ$$

$$E''_{oc} = E''_{Th} = 21 \text{ V} = 210 \text{ V } \angle 0^\circ$$

I_{sc} :

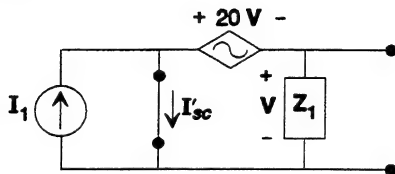

$$I'_{sc} = I_1$$

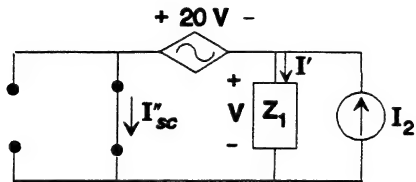

$$20 \text{ V} = V \therefore V = 0 \text{ V}$$

$$\text{and } I' = 0 \text{ A}$$

$$\therefore I''_{sc} = I_2$$


$$I_{sc} = I'_{sc} + I''_{sc} = 3 \text{ mA } \angle 0^\circ$$

$$E_{oc} = E'_{oc} + E''_{oc} = 315 \text{ V } \angle 0^\circ = E_{Th}$$

$$Z_{Th} = \frac{E_{oc}}{I_{sc}} = \frac{315 \text{ V } \angle 0^\circ}{3 \text{ mA } \angle 0^\circ} = 105 \text{ k}\Omega \angle 0^\circ$$

26. a. From Problem 12(a): $Z_N = Z_{Th} = 1.92 \Omega + j1.44 \Omega = 2.4 \Omega \angle 36.87^\circ$

I_N :

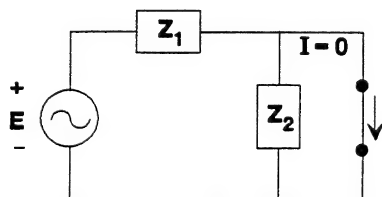


$$Z_1 = 3 \Omega \angle 0^\circ, Z_2 = 4 \Omega \angle 90^\circ$$

$$I_{sc} = I_N = \frac{E}{Z_1} = \frac{100 \text{ V} \angle 0^\circ}{3 \Omega \angle 0^\circ} = 33.33 \text{ A} \angle 0^\circ$$

- b. From Problem 12(b): $Z_N = Z_{Th} = 5.263 \text{ k}\Omega \angle 74.741^\circ = 1.385 \text{ k}\Omega + j6.923 \text{ k}\Omega$

I_N :

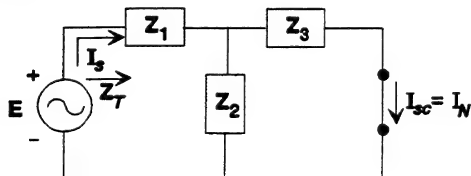

$$Z_1 = 2 \text{ k}\Omega \angle 0^\circ, Z_2 = 3 \text{ k}\Omega \angle -90^\circ$$

$$Z_3 = 6 \text{ k}\Omega \angle 90^\circ$$


$$\begin{aligned} Z_T &= Z_1 + Z_2 \parallel Z_3 \\ &= 2 \text{ k}\Omega + 3 \text{ k}\Omega \angle -90^\circ \parallel 6 \text{ k}\Omega \angle 90^\circ \\ &= 2 \text{ k}\Omega + 6 \text{ k}\Omega \angle -90^\circ \\ &= 2 \text{ k}\Omega - j6 \text{ k}\Omega \\ &= 6.325 \text{ k}\Omega \angle -71.565^\circ \end{aligned}$$

$$\begin{aligned} I_s &= \frac{E}{Z_T} = \frac{20 \text{ V} \angle 0^\circ}{6.325 \text{ k}\Omega \angle -71.565^\circ} \\ &= 3.162 \text{ mA} \angle 71.565^\circ \end{aligned}$$

$$\begin{aligned} I_{sc} = I_N &= \frac{Z_2 I_s}{Z_2 + Z_3} = \frac{(3 \text{ k}\Omega \angle -90^\circ)(3.162 \text{ mA} \angle 71.565^\circ)}{-j3 \text{ k}\Omega + j6 \text{ k}\Omega} \\ &= \frac{9.486 \text{ mA} \angle -18.435^\circ}{3 \angle 90^\circ} = 3.162 \text{ mA} \angle -108.435^\circ \end{aligned}$$

28. a. From Problem 14(a): $Z_N = Z_{Th} = 4.997 \Omega \angle -38.663^\circ$

I_N : Superposition:

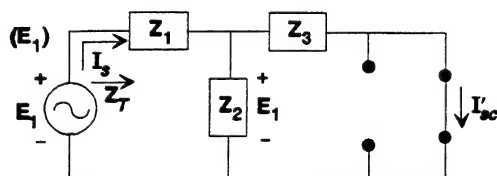

$$\begin{aligned} Z_T &= Z_1 + Z_2 \parallel Z_3 \\ &= 10 \Omega + 8 \Omega \angle 90^\circ \parallel 8 \Omega \angle -90^\circ \\ &= 10 \Omega + \frac{64 \Omega \angle 0^\circ}{0} \\ &= \text{very large impedance} \end{aligned}$$


$$I_s = \frac{E}{Z_T} = 0 \text{ A}$$

$$\text{and } V_{Z_1} = 0 \text{ V}$$

$$\text{with } V_{Z_2} = V_{Z_3} = E_1 = 120 \text{ V} \angle 0^\circ$$


$$\begin{aligned} \text{so that } I'_{sc} &= \frac{E_1}{Z_3} = \frac{120 \text{ V} \angle 0^\circ}{8 \Omega \angle -90^\circ} \\ &= 15 \text{ A} \angle 90^\circ \end{aligned}$$

(I)

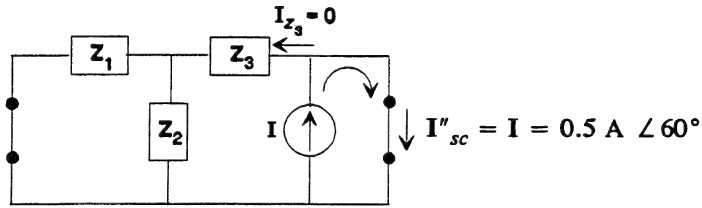

$$\begin{aligned} I_N &= I'_{sc} + I''_{sc} = +j15 \text{ A} + 0.5 \text{ A} \angle 60^\circ = +j15 \text{ A} + 0.25 \text{ A} + j0.433 \text{ A} \\ &= 0.25 \text{ A} + j15.433 \text{ A} = 15.435 \text{ A} \angle 89.072^\circ \end{aligned}$$

- b. From Problem 14(b): $Z_N = Z_{Th} = 10 \Omega - j10 \Omega = 14.142 \Omega \angle -45^\circ$

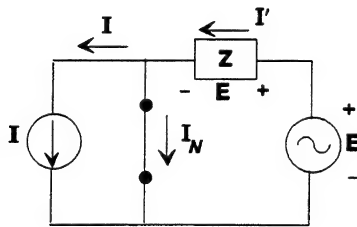
 I_N :

$$\begin{aligned} I_N &= I' - I \\ &= \frac{E}{Z} - I \\ &= \frac{20 \text{ V} \angle 40^\circ}{14.142 \Omega \angle -45^\circ} - 0.6 \text{ A} \angle 90^\circ \\ &= 1.414 \text{ A} \angle 85^\circ - j0.6 \text{ A} \\ &= 0.123 \text{ A} + j1.409 \text{ A} - j0.6 \text{ A} \\ &= 0.123 \text{ A} + j0.809 \text{ A} \\ &= 0.818 \text{ A} \angle 81.355^\circ \end{aligned}$$

30. a. Note Problem 15(a): $Z_N = Z_{Th} = 4 \Omega \angle 90^\circ$


 I_N :

DC

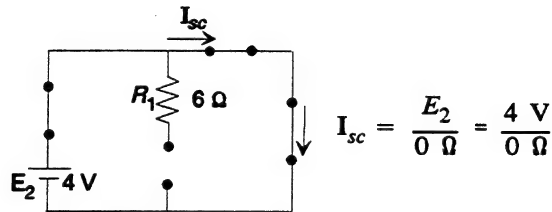

$$I_{sc} = \frac{E_2}{0 \Omega} = \frac{4 \text{ V}}{0 \Omega}$$

AC

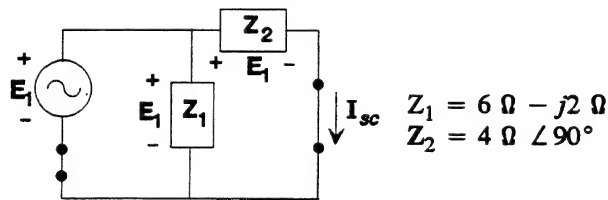


$$\begin{aligned} Z_1 &= 6 \Omega - j2 \Omega \\ Z_2 &= 4 \Omega \angle 90^\circ \end{aligned}$$

$$I_{sc} = \frac{E_1}{Z_2} = \frac{10 \text{ V} \angle 0^\circ}{4 \Omega \angle 90^\circ} = 2.5 \text{ A} \angle -90^\circ$$


$$I_N = \frac{4 \text{ V}}{0 \Omega} + 2.5 \text{ A} \angle -90^\circ \quad (\text{dc: } E_{Th} = I_N Z_N = \frac{4 \text{ V}}{(0 \Omega)} (0 \Omega) = 4 \text{ V})$$

b.

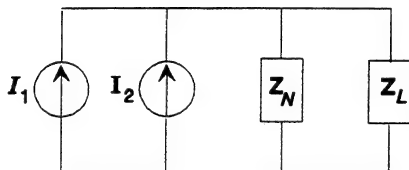

$$\begin{aligned} Z_N &= 4 \Omega \angle 90^\circ \\ Z_L &= 8 \Omega \angle 0^\circ \end{aligned}$$

DC:

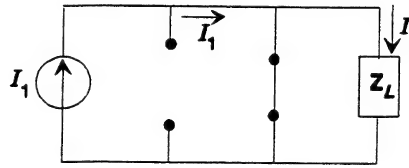

(CDR)

$$I = \frac{(0 \Omega) I_1}{0 \Omega + 8 \Omega} = \frac{(0 \Omega) \left(\frac{4 \text{ V}}{0 \Omega} \right)}{0 \Omega + 8 \Omega} = \frac{4 \text{ V}}{8 \Omega} = 0.5 \text{ A}$$

as obtained in Problem 15

AC:

$$I = \frac{Z_N(I_2)}{Z_N + Z_L} = \frac{(4 \Omega \angle 90^\circ)(2.5 \text{ A} \angle -90^\circ)}{+j4 \Omega + 8 \Omega}$$

$$= \frac{10 \text{ V} \angle 0^\circ}{8.944 \Omega \angle 26.565^\circ} = 1.118 \text{ A} \angle -26.565^\circ \text{ as obtained in Problem 15}$$


$$I_{8\Omega} = 0.5 \text{ A} + 1.118 \text{ A} \angle -26.565^\circ$$

(dc) (ac)

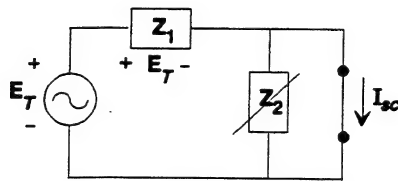32. a. Note Problem 17(a): $Z_N = Z_{Th} = 4.472 \text{ k}\Omega \angle -26.565^\circ$

Using the same source conversion: $E_1 = 50 \text{ V} \angle 0^\circ$

Defining $E_T = E_1 + E = 50 \text{ V} \angle 0^\circ + 20 \text{ V} \angle 0^\circ = 70 \text{ V} \angle 0^\circ$



$$Z_1 = 10 \text{ k}\Omega \angle 0^\circ$$

$$Z_2 = 5 \text{ k}\Omega - j5 \text{ k}\Omega = 7.071 \text{ k}\Omega \angle -45^\circ$$

$$I_{sc} = \frac{E_T}{Z_1} = \frac{70 \text{ V} \angle 0^\circ}{10 \text{ k}\Omega \angle 0^\circ} = 7 \text{ mA} \angle 0^\circ$$


$$I_N = I_{sc} = 7 \text{ mA} \angle 0^\circ$$

b. $I = \frac{Z_N(I_N)}{Z_N + Z_L} = \frac{(4.472 \text{ k}\Omega \angle -26.565^\circ)(7 \text{ mA} \angle 0^\circ)}{4.472 \text{ k}\Omega \angle -26.565^\circ + 5 \text{ k}\Omega \angle 90^\circ}$

$$= \frac{31.30 \text{ mA} \angle -26.565^\circ}{4 - j2 + j5} = \frac{31.30 \text{ mA} \angle -26.565^\circ}{4 + j3}$$

$$= \frac{31.30 \text{ mA} \angle -26.565^\circ}{5 \angle 36.87^\circ} = 6.26 \text{ mA} \angle 63.435^\circ \text{ as obtained in Problem 17.}$$

34. Z_N :

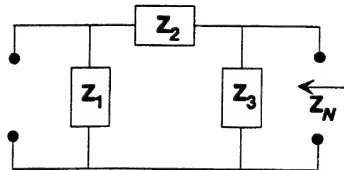

$$Z_1 = 40 \text{ k}\Omega \angle 0^\circ, Z_2 = 0.2 \text{ k}\Omega \angle -90^\circ$$


$$Z_3 = 5 \text{ k}\Omega \angle 0^\circ$$

$$Z_N = Z_3 \parallel (Z_1 + Z_2)$$

$$= 5 \text{ k}\Omega \angle 0^\circ \parallel (40 \text{ k}\Omega - j0.2 \text{ k}\Omega)$$


$$= 4.44 \text{ k}\Omega \angle -0.031^\circ$$

I_N :

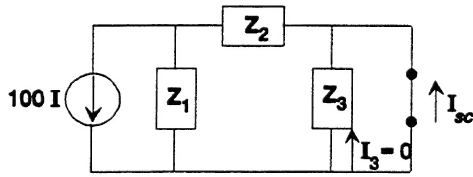

$$\begin{aligned} I_N = I_{sc} &= \frac{Z_1(100 I)}{Z_1 + Z_2} \\ &= \frac{(40 \text{ k}\Omega \angle 0^\circ)(100 I)}{40 \text{ k}\Omega \angle -0.286^\circ} \\ &= 100 I \angle 0.286^\circ \end{aligned}$$


36. Z_N :

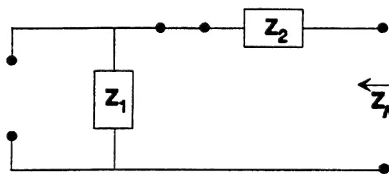

$$\begin{aligned} Z_1 &= 20 \text{ k}\Omega \angle 0^\circ, Z_2 = 5 \text{ k}\Omega \angle 0^\circ \\ V &= 10 \text{ V} \angle 0^\circ, \mu = 20, h = 100 \\ I &= 1 \text{ mA} \angle 0^\circ \end{aligned}$$


$$Z_N = Z_1 + Z_2 = 25 \text{ k}\Omega \angle 0^\circ$$

$I_N (hI)$

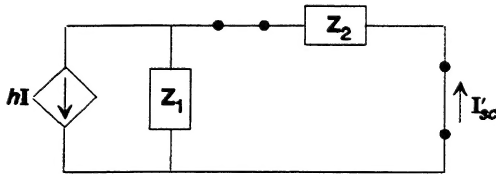

$$\begin{aligned} I'_{sc} &= \frac{Z_1(hI)}{Z_1 + Z_2} \\ &= \frac{(20 \text{ k}\Omega \angle 0^\circ)(hI)}{20 \text{ k}\Omega \angle 0^\circ + 5 \text{ k}\Omega \angle 0^\circ} \\ &= 80 \text{ mA} \angle 0^\circ \end{aligned}$$


(μV)

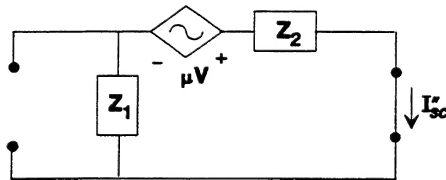

$$\begin{aligned} I''_{sc} &= \frac{\mu V}{Z_1 + Z_2} = \frac{(20)(10 \text{ V} \angle 0^\circ)}{25 \text{ k}\Omega} \\ &= 8 \text{ mA} \angle 0^\circ \end{aligned}$$

$$I_N (\text{direction of } I'_{sc}) = I'_{sc} - I''_{sc} = 80 \text{ mA} \angle 0^\circ - 8 \text{ mA} \angle 0^\circ = 72 \text{ mA} \angle 0^\circ$$

38.

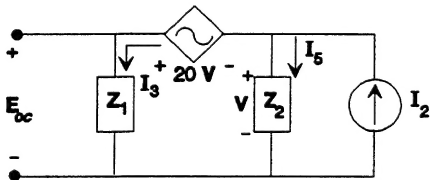


$$\begin{aligned} Z_1 &= 2 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 5 \text{ k}\Omega \angle 0^\circ \end{aligned}$$

$$\begin{aligned} I_2 &= I_3 + I_5 \\ V &= I_5 Z_2 = (I_2 - I_3) Z_2 \\ E_{oc} = E_{Th} &= 21 \text{ V} = 21(I_2 - I_3) Z_2 \\ &= 21 \left[I_2 - \frac{E_{oc}}{Z_1} \right] Z_2 \\ E_{oc} \left[1 + 21 \frac{Z_2}{Z_1} \right] &= 21 Z_2 I_2 \end{aligned}$$

$$E_{oc} = \frac{21 Z_2 I_2}{1 + 21 \frac{Z_2}{Z_1}} = \frac{21(5 \text{ k}\Omega \angle 0^\circ)(2 \text{ mA} \angle 0^\circ)}{1 + 21 \left[\frac{5 \text{ k}\Omega \angle 0^\circ}{2 \text{ k}\Omega \angle 0^\circ} \right]}$$
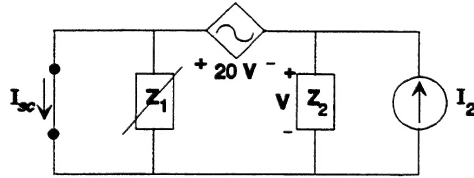
$$E_{Th} = E_{oc} = 3.925 \text{ V} \angle 0^\circ$$




$$20 \text{ V} \neq -V \therefore V = 0$$

$$\text{and } I_{sc} = I_2 = I_N = 2 \text{ mA} \angle 0^\circ$$

$$Z_N = \frac{E_{oc}}{I_{sc}} = \frac{3.925 \text{ V} \angle 0^\circ}{2 \text{ mA} \angle 0^\circ} = 1.9625 \text{ k}\Omega$$

40. a. Z_{Th} :

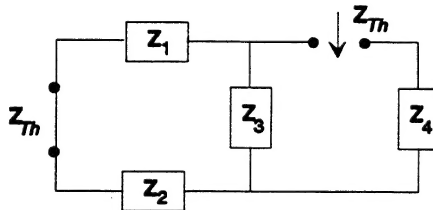

$$Z_1 = 4 \Omega \angle 90^\circ, Z_2 = 10 \Omega \angle 0^\circ$$

$$Z_3 = 5 \Omega \angle -90^\circ, Z_4 = 6 \Omega \angle -90^\circ$$

$$E = 60 \text{ V} \angle 60^\circ$$


$$Z_{Th} = Z_4 + Z_3 \parallel (Z_1 + Z_2) = -j6 \Omega + (5 \Omega \angle -90^\circ) \parallel (10 \Omega + j4 \Omega)$$

$$= 2.475 \Omega - j4.754 \Omega$$

$$= 11.035 \Omega \angle -77.03^\circ$$

$$Z_L = 11.035 \Omega \angle 77.03^\circ$$

E_{Th} :

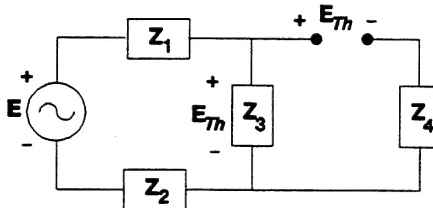


$$E_{Th} = \frac{Z_3(E)}{Z_3 + Z_1 + Z_2}$$

$$= \frac{(5 \Omega \angle -90^\circ)(60 \text{ V} \angle 60^\circ)}{-j5 \Omega + j4 \Omega + 10 \Omega}$$

$$= 29.85 \text{ V} \angle -24.29^\circ$$

$$P_{\max} = E_{Th}^2 / 4R_{Th} = (29.85 \text{ V})^2 / 4(2.475 \Omega) = 90 \text{ W}$$

b.

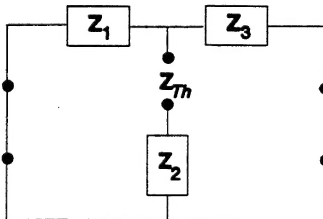

$$Z_1 = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ$$


$$Z_2 = -j8 \Omega$$

$$Z_3 = 12 \Omega + j9 \Omega$$

$$Z_{Th} = Z_2 + Z_1 \parallel Z_3 = -j8 \Omega + (5 \Omega \angle 53.13^\circ) \parallel (15 \Omega \angle 36.87^\circ)$$

$$= 5.71 \Omega \angle -64.30^\circ = 2.475 \Omega - j5.143 \Omega$$
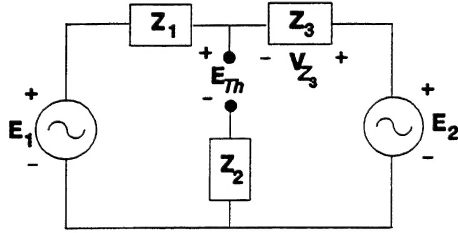
$$Z_L = 5.71 \Omega \angle 64.30^\circ = 2.475 \Omega + j5.143 \Omega$$



$$E_{Th} + V_{Z_3} - E_2 = 0$$

$$E_{Th} = E_2 - V_{Z_3}$$

$$V_{Z_3} = \frac{Z_3(E_2 - E_1)}{Z_3 + Z_1} = 168.97 \text{ V } \angle 112.53^\circ$$

$$E_{Th} = E_2 - V_{Z_3} = 200 \text{ V } \angle 90^\circ - 168.97 \text{ V } \angle 112.53^\circ = 78.24 \text{ V } \angle 34.16^\circ$$

$$P_{\max} = E_{Th}^2 / 4R_{Th} = (78.24 \text{ V})^2 / 4(2.475 \Omega) = 618.33 \text{ W}$$


42. a. $Z_{Th} = 4 \Omega \angle 90^\circ$ (Problem 15(a))
 $Z_L = 4 \text{ k}\Omega \angle -90^\circ$

b. Since load purely reactive P_{\max} undefined ($P_{\max} = \frac{E_{Th}^2}{4R_{Th}}$, $R_{Th} = 0 \Omega$)

44. a. Problem 17(a):
 $Z_{Th} = 4.472 \text{ k}\Omega \angle -26.565^\circ = 4 \text{ k}\Omega - j2 \text{ k}\Omega$
 $Z_L = 4 \text{ k}\Omega + j2 \text{ k}\Omega$
 $E_{Th} = 31.31 \text{ V } \angle -26.565^\circ$

b. $P_{\max} = E_{Th}^2 / 4R_{Th} = (31.31 \text{ V})^2 / 4(4 \text{ k}\Omega) = 61.27 \text{ mW}$

46. a. Z_{Th} :

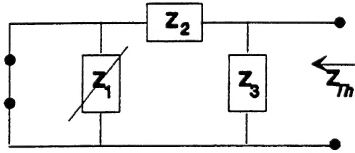

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(10 \text{ kHz})(3.98 \text{ nF})} \cong 4 \text{ k}\Omega$$

$$X_L = 2\pi fL = 2\pi(10 \text{ kHz})(31.8 \text{ mH}) \cong 2 \text{ k}\Omega$$

$$Z_1 = 1 \text{ k}\Omega \angle 0^\circ, Z_2 = 2 \text{ k}\Omega \angle 90^\circ$$

$$Z_3 = 4 \text{ k}\Omega \angle -90^\circ$$


$$Z_{Th} = Z_2 \parallel Z_3 = (2 \text{ k}\Omega \angle 90^\circ) \parallel (4 \text{ k}\Omega \angle -90^\circ) = 4 \text{ k}\Omega \angle 90^\circ, Z_L = 4 \text{ k}\Omega \angle -90^\circ$$

$$X_C = \frac{1}{2\pi fC} = 4 \text{ k}\Omega, C = \frac{1}{2\pi fX_C} = \frac{1}{2\pi(10 \text{ kHz})(4 \text{ k}\Omega)} = 3.97 \text{ nF}$$

b. $R_{Th} = 0 \Omega \therefore R_L = 0 \Omega$

c. Undefined since $P_{\max} = E_{Th}^2 / 4R_{Th}$ and $R_{Th} = 0 \Omega$

48. a.

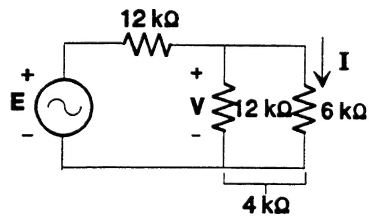


$$V = \frac{4 \text{ k}\Omega(E)}{4 \text{ k}\Omega + 12 \text{ k}\Omega} = \frac{1}{4}(20 \text{ V } \angle 0^\circ)$$

$$= 5 \text{ V } \angle 0^\circ$$

$$I = \frac{5 \text{ V } \angle 0^\circ}{6 \text{ k}\Omega} = 0.833 \text{ mA } \angle 0^\circ$$

b.

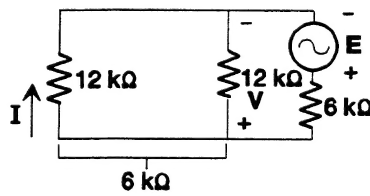

$$V = \frac{6 \text{ k}\Omega(E)}{6 \text{ k}\Omega + 6 \text{ k}\Omega} = \frac{1}{2}(20 \text{ V } \angle 0^\circ)$$

$$= 10 \text{ V } \angle 0^\circ$$

$$I = \frac{10 \text{ V } \angle 0^\circ}{12 \text{ k}\Omega} = 0.833 \text{ mA } \angle 0^\circ$$